
MyElectronicProjects Documentation

Release 0.0.0

ponty

December 03, 2012

CONTENTS

1	About	2
2	Stripboard design	3
3	AC mains alarm	4
3.1	Pins	4
3.2	Schematic	4
3.3	Board	5
3.4	Partlist	6
3.5	3D view	6
3.6	Sources	8
4	audio amplifier	9
4.1	Schematic	9
4.2	Board	10
4.3	Partlist	11
4.4	3D view	12
4.5	Sources	14
5	AVR ISP Header adapter	15
5.1	Schematic	15
5.2	Board	16
5.3	Partlist	16
5.4	3D view	17
5.5	Sources	19
6	DAPA AVR programmer	20
6.1	Test on Ubuntu	20
6.2	Image	20
6.3	Schematic	21
6.4	Partlist	21
6.5	Sources	21
7	FM transmitter	22
8	FTDI cable	23
8.1	Sources	23
9	function generator	24
9.1	Schematic	24
10	Garmin eTrex data cable	25
10.1	Images	25
10.2	Sources	26

11 IR amplifier	27
11.1 Schematic	27
11.2 Board	28
11.3 Partlist	29
11.4 3D view	29
12 IrDA port	32
12.1 Schematic	32
12.2 Board	32
13 LCD module	33
13.1 Schematic	33
13.2 Board	34
14 Lightning detector	35
14.1 Schematic	35
14.2 Sources	35
15 LIRC serial receiver	36
15.1 Schematic	36
15.2 Board	37
15.3 Partlist	38
15.4 3D view	38
16 logic probe	41
17 Nokia adapter	42
17.1 Sources	42
18 Op-amp module	43
18.1 Schematic	43
18.2 Board	44
18.3 Partlist	44
18.4 3D view	45
19 outlet tester	48
19.1 Schematic	48
19.2 Board	49
19.3 Partlist	50
19.4 3D view	51
19.5 Sources	53
20 Parallel port monitor	54
20.1 Images	54
20.2 Schematic	56
20.3 Board	57
20.4 Partlist	58
20.5 3D view	59
20.6 Sources	61
21 PIC ICSP programmer	62
21.1 Schematic	62
21.2 Board	63
21.3 Sources	63
22 Pong	64
22.1 Schematic	64
22.2 Board	65
22.3 Partlist	66
22.4 3D view	66

22.5	Sources	69
23	power supply	70
23.1	Schematic	70
23.2	Board	70
24	Preamplifier	71
24.1	Schematic	71
24.2	Board	72
24.3	Partlist	72
24.4	3D view	73
24.5	Sources	75
25	propic2 PIC programmer	77
26	Serial port 1wire adapter	80
27	Serial port loopback plug	81
27.1	Images	81
27.2	Sources	81
28	serial port monitor	83
28.1	Schematic	83
28.2	Board	84
28.3	Partlist	85
28.4	3D view	85
28.5	Images	87
29	standby killer	89
29.1	Schematic	89
29.2	Board	90
29.3	Sources	90
30	STK200 AVR programmer	91
30.1	Test on Ubuntu	91
30.2	Image	91
30.3	Schematic	93
30.4	Board	94
30.5	Partlist	95
30.6	3D view	96
30.7	Sources	98
31	USB 1wire hub	99
31.1	Schematic	100
31.2	Board	101
31.3	Partlist	102
31.4	3D view	103
32	USB trickle charger	106
32.1	Power dissipation	106
32.2	Charge time	106
32.3	Schematic	107
32.4	Sources	107
33	USB LED	108
34	USBasp AVR programmer	109
34.1	V-USB hardware recommendation	109
34.2	Makefile	110
34.3	Test on Ubuntu	110

34.4	Schematic	111
34.5	Board	112
34.6	Partlist	113
34.7	3D view	114
34.8	Reset	116
34.9	Sources	117
35	Wire bending tool	118
35.1	Image	118
35.2	Board	118
35.3	3D view	119
36	Wire detector	121
36.1	Schematic	121
36.2	Board	122
36.3	Partlist	122
36.4	3D view	123
36.5	Sources	125

MyElectronicProjects

Date December 03, 2012

PDF MyElectronicProjects.pdf

ABOUT

Hobby electronic projects built by me.

Most of them are built on stripboard.

Links:

- home: <https://github.com/ponty/MyElectronicProjects>
- documentation: <http://ponty.github.com/MyElectronicProjects>

Design tool: [EAGLE Light Edition](#)

STRIPBOARD DESIGN

Stripboard design representation in eagle:

- holes: copper should be cut or drilled here
- SMD: through-hole component, legs are drawn on top layer
- top layer: wires
- lines on documentation layer: wires
- bottom layer: original parallel strips of copper, only those are drawn, which are used for connection
- via: soldering points

Some components have no 3D view in the documentation.

AC MAINS ALARM


Status: OK

This device makes alarm sound periodically when the near cable has AC signal. In debug mode it can be used as AC mains detector.

3.1 Pins




board pin	AVR pin	Arduino pin
in	PC3	A3
speaker	PB1	D9
debug in	PC0	A0
debug LED	PC5	A5

3.2 Schematic

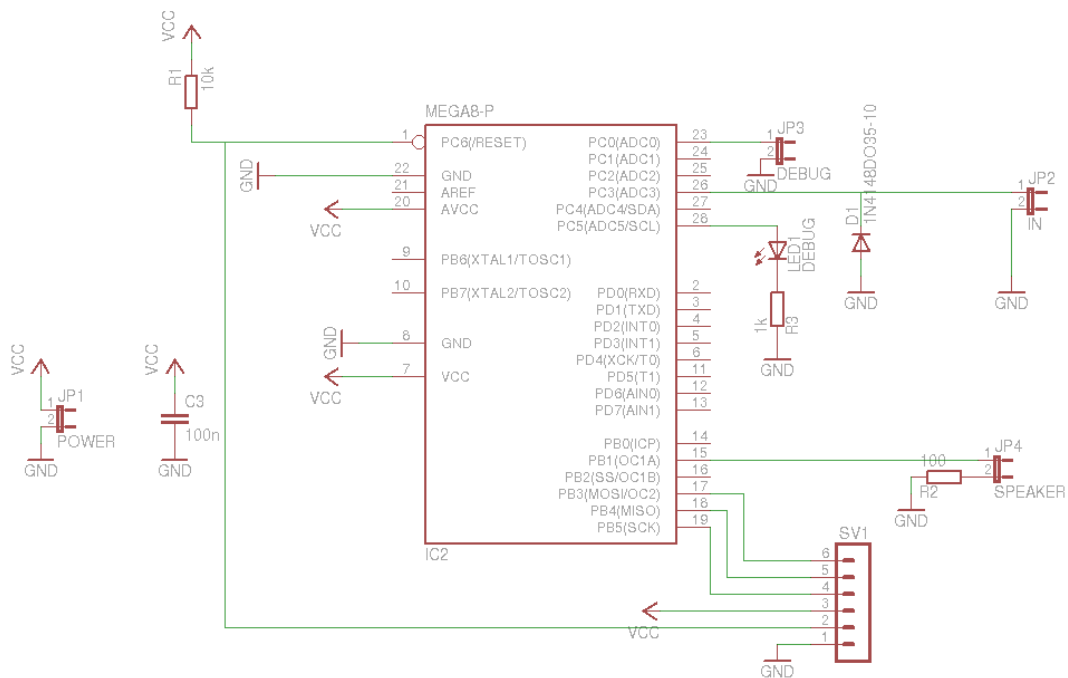

3.3 Board

Normal, bottom mirrored, wires only:

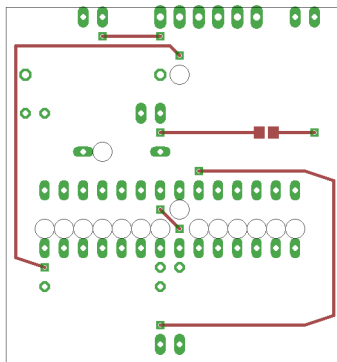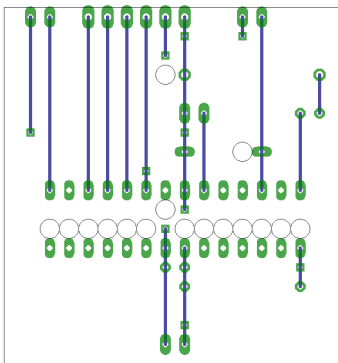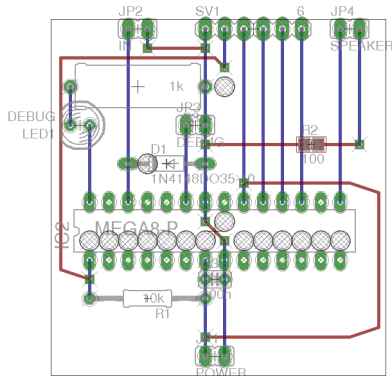


3.4 Partlist

Table 3.1:


part	value	position
C3	100n	(1.45 0.4)
D1	1N4148DO35-10	(1.2 1)
IC2	MEGA8-P	(1.45 0.65)
JP1	POWER	(1.45 0)
JP2	IN	(1.05 1.7)
JP3	DEBUG	(1.35 1.2)
JP4	SPEAKER	(2.15 1.7)
LED1	DEBUG	(0.75 1.2)
R1	10k	(1.1 0.3)
R2	100	(1.95 1.1)
R3	1k	(1.05 1.4)
SV1		(1.65 1.7)

3.5 3D view


3.5.1 Front

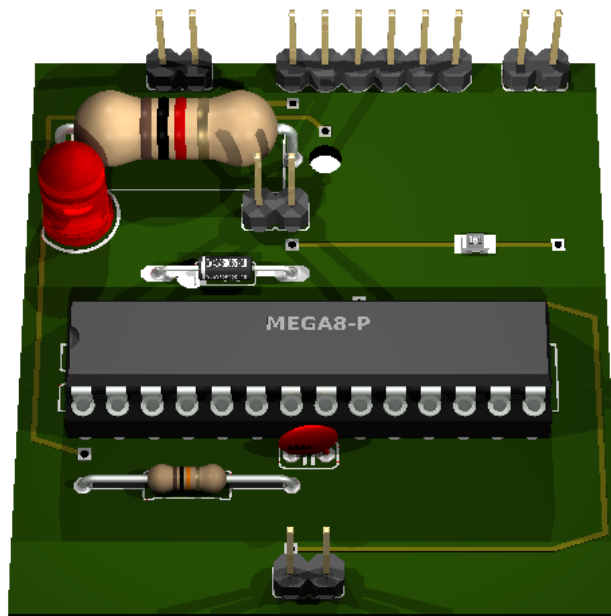


3.5.2 Right side

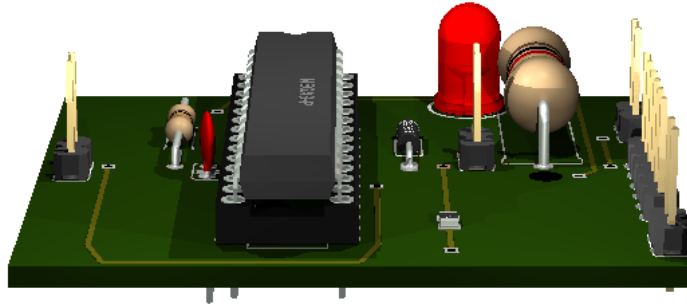

3.5.3 Left side

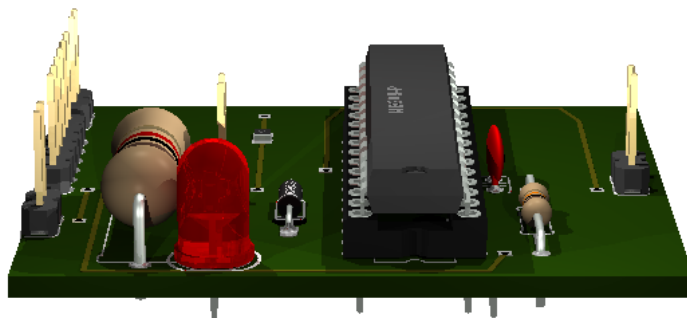

3.5.4 Bottom

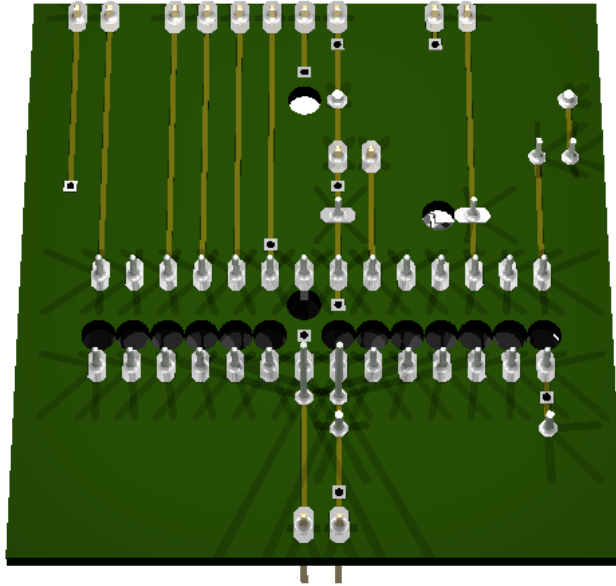

3.6 Sources


Based on this design: http://www.edn.com/article/511304-Detect_live_ac_mains_lines.php

AUDIO AMPLIFIER

Status: under construction




It is used for ...

4.1 Schematic

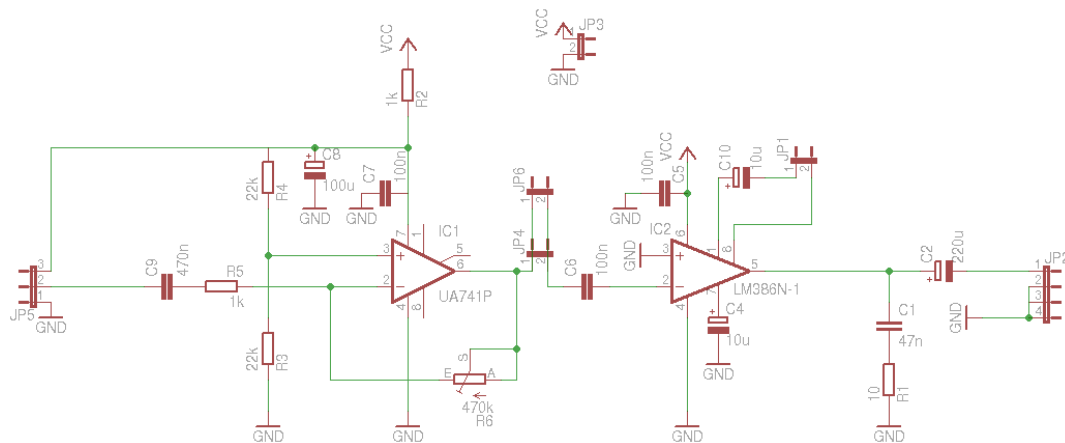

4.2 Board

Normal, bottom mirrored, wires only:

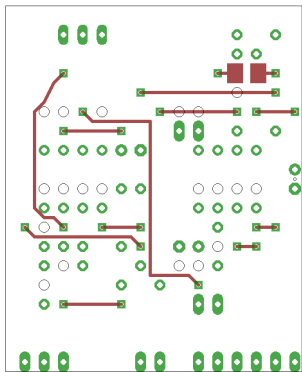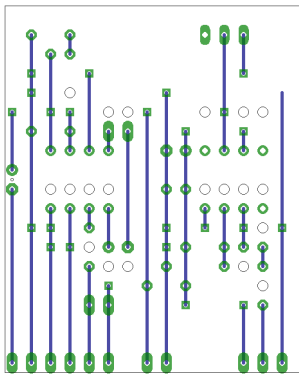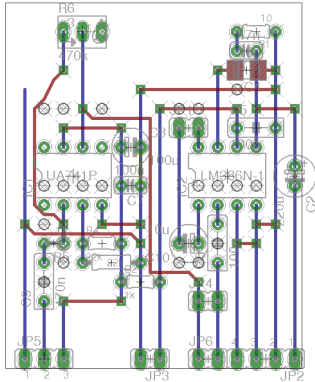


4.3 Partlist

Table 4.1:


part	value	position
C1	47n	(1.45 1.7)
C2	220u	(1.7 1.05)
C4	10u	(1.45 1.6)
C5	100n	(1.5 1.3)
C6	100n	(1.3 0.7)
C7	100n	(0.85 1)
C8	100u	(0.85 1.2)
C9	470n	(0.4 0.5)
C10	10u	(1.15 0.7)
IC1	UA741P	(0.55 1.05)
IC2	LM386N-1	(1.35 1.05)
JP1		(1.15 1.3)
JP2		(1.55 0.1)
JP3		(0.95 0.1)
JP4		(1.25 0.4)
JP5		(0.4 0.1)
JP6		(1.25 0.1)
R1	10	(1.5 1.8)
R2	1k	(0.9 0.5)
R3	22k	(0.75 0.6)
R4	22k	(0.7 0.7)
R5	1k	(0.45 0.7)
R6	470k	(0.6 1.8)

4.4 3D view


4.4.1 Front

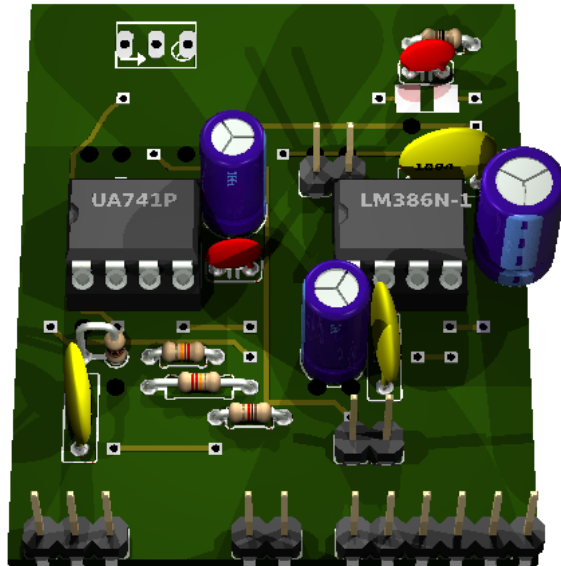


4.4.2 Right side

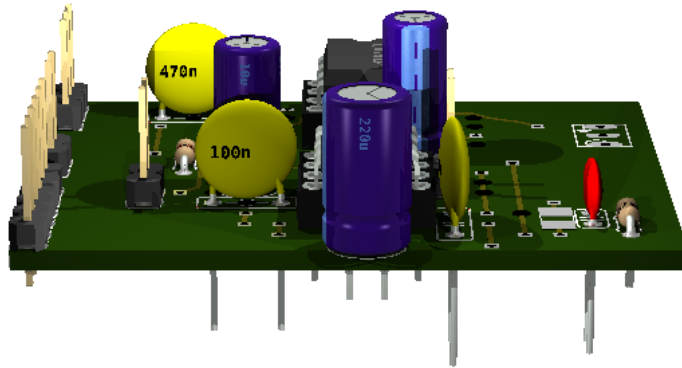

4.4.3 Left side

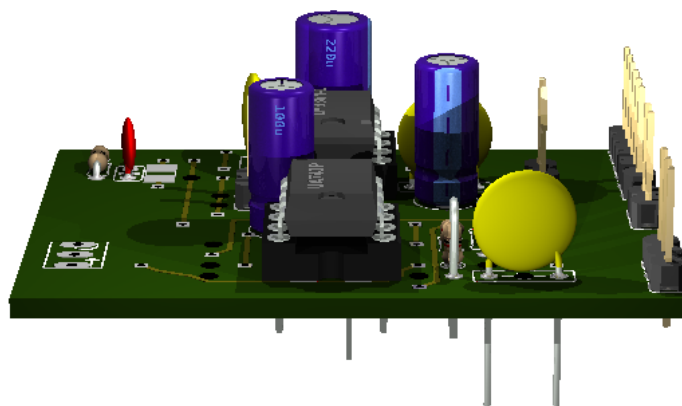

4.4.4 Bottom

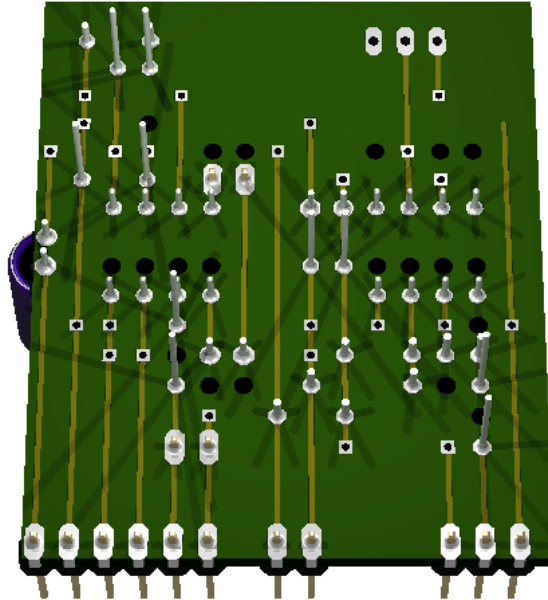

4.5 Sources


original design

AVR ISP HEADER ADAPTER

Status: OK


This board converts the AVR ISP 10 pin Header to a custom 6 pin header, which is easy to add to a stripboard with Atmega8 pin compatible microcontroller.

5.1 Schematic

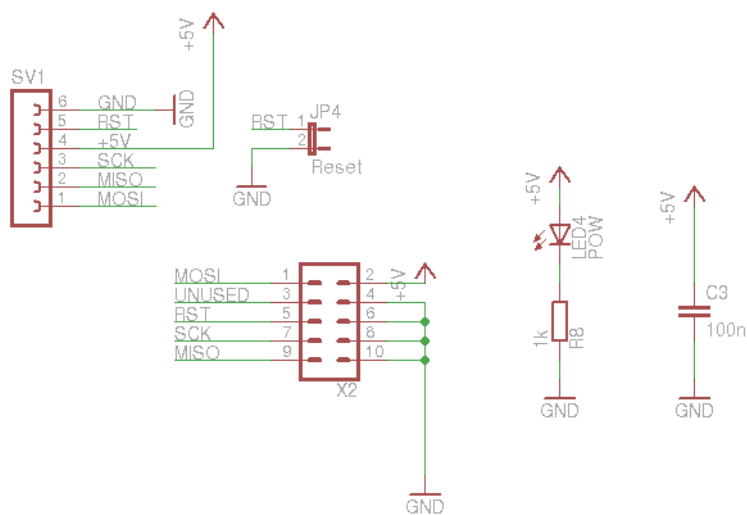

5.2 Board

Normal, bottom mirrored, wires only:

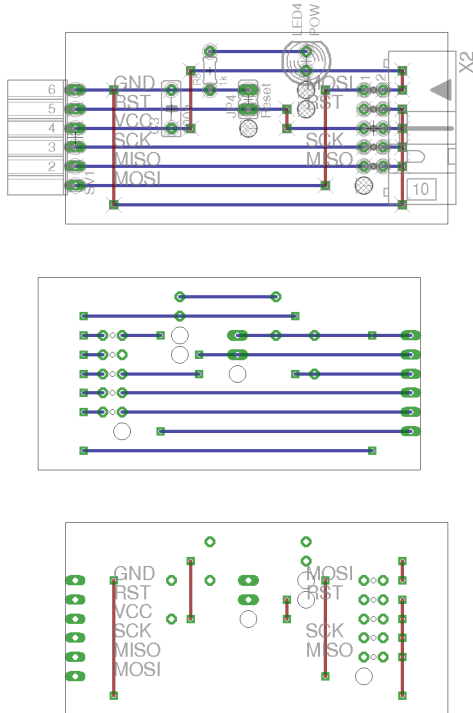


5.3 Partlist

Table 5.1:


part	value	position
C3	100n	(0.6 0.7)
JP4	Reset	(1 0.75)
LED4	POW	(1.3 0.95)
R8	1k	(0.8 0.9)
SV1		(0.1 0.55)
X2		(1.65 0.6)

5.4 3D view


5.4.1 Front

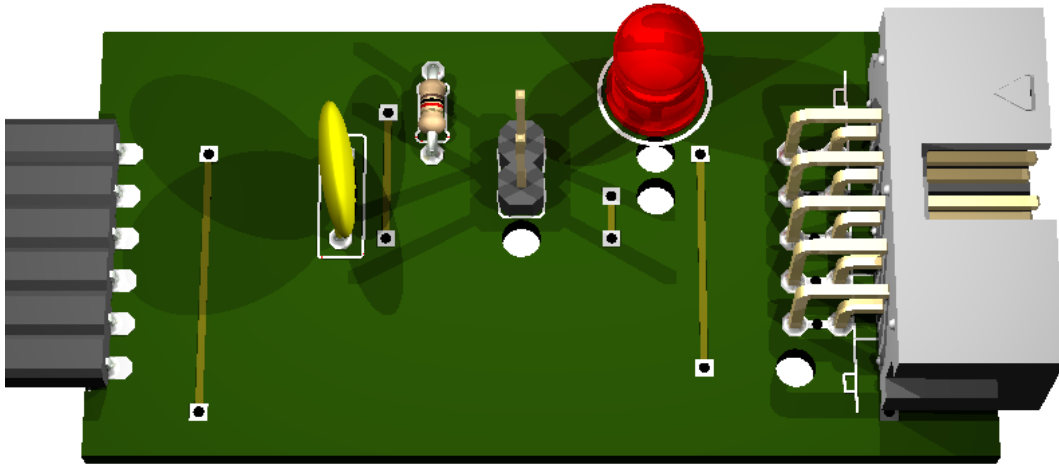


5.4.2 Right side

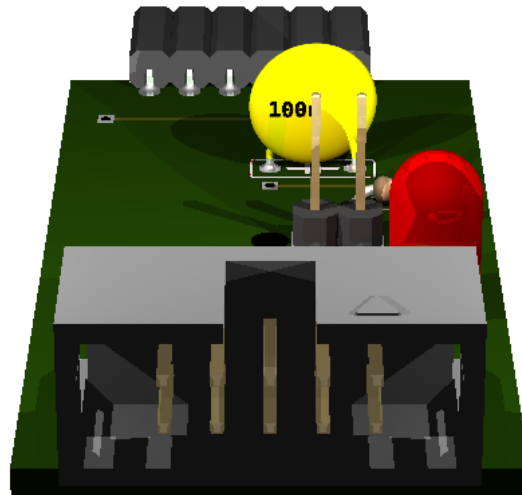

5.4.3 Left side

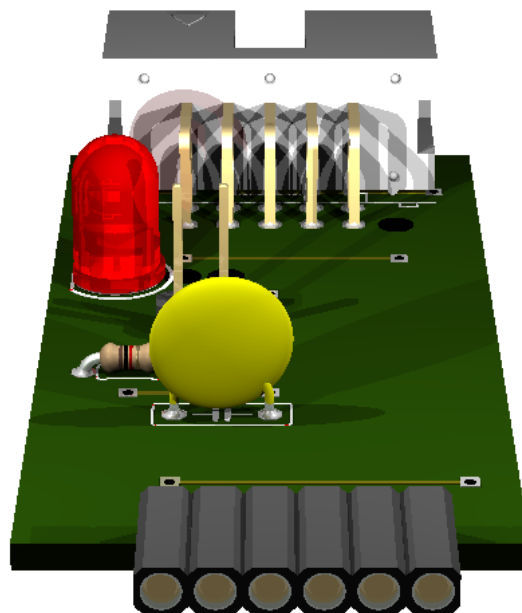

5.4.4 Bottom

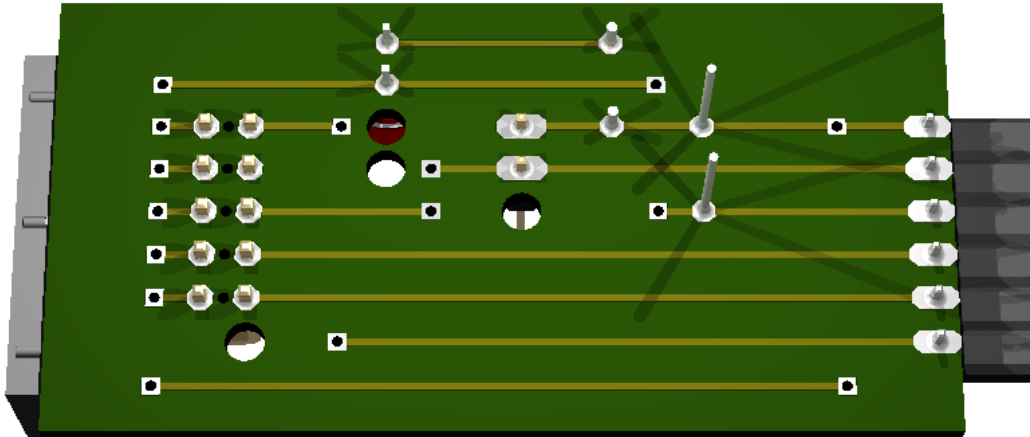

5.5 Sources

AVR ISP Header Pinouts

DAPA AVR PROGRAMMER

Status: OK

It is used for programming AVR controller and Arduino compatible boards using the parallel port.

6.1 Test on Ubuntu

checking:

```
$ avrdude -patmega88 -cdapa
```

```
avrdude: AVR device initialized and ready to accept instructions
```


```
Reading | ##### | 100% 0.00s
```

```
avrdude: Device signature = 0x1e930a
```


```
avrdude: safemode: Fuses OK
```

```
avrdude done. Thank you.
```

6.2 Image

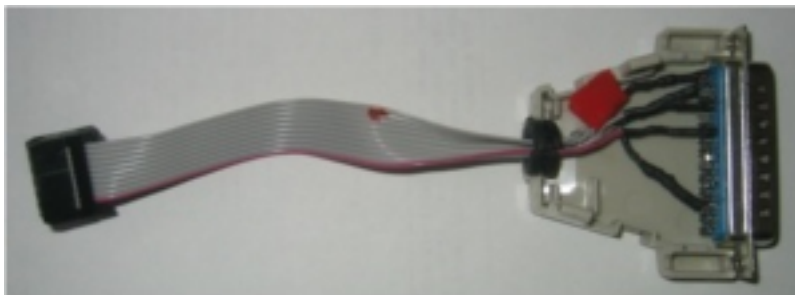

6.3 Schematic

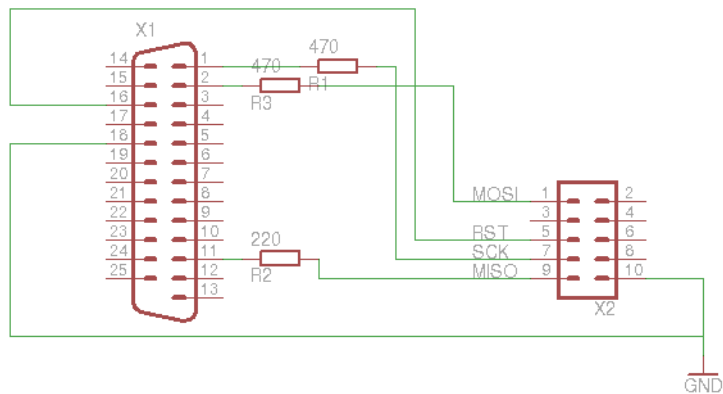

6.4 Partlist

Table 6.1:

part	value
R1	470
R2	220
R3	470
X1	
X2	

6.5 Sources

original design

Parallel port specification

AVR ISP Header Pinouts

FM TRANSMITTER

Status: OK

source: <http://rclindia.tripod.com/trans.html>

FTDI CABLE

Status: OK

Special cable.

connections:

FTDI pin	signal	color	6p4c (RJ14) pin
1	gnd	red	4
2	cts		
3	5v	green	3
4	rx	yellow	2
5	tx	black	5
6	rts		

standard color code is reversed

8.1 Sources

[RJ14 pinout](#)

[RJ14 wiring details](#)


FUNCTION GENERATOR

Status: OK

Power input:

1x AC (9-15V) or 2x DC (9-20V)

9.1 Schematic

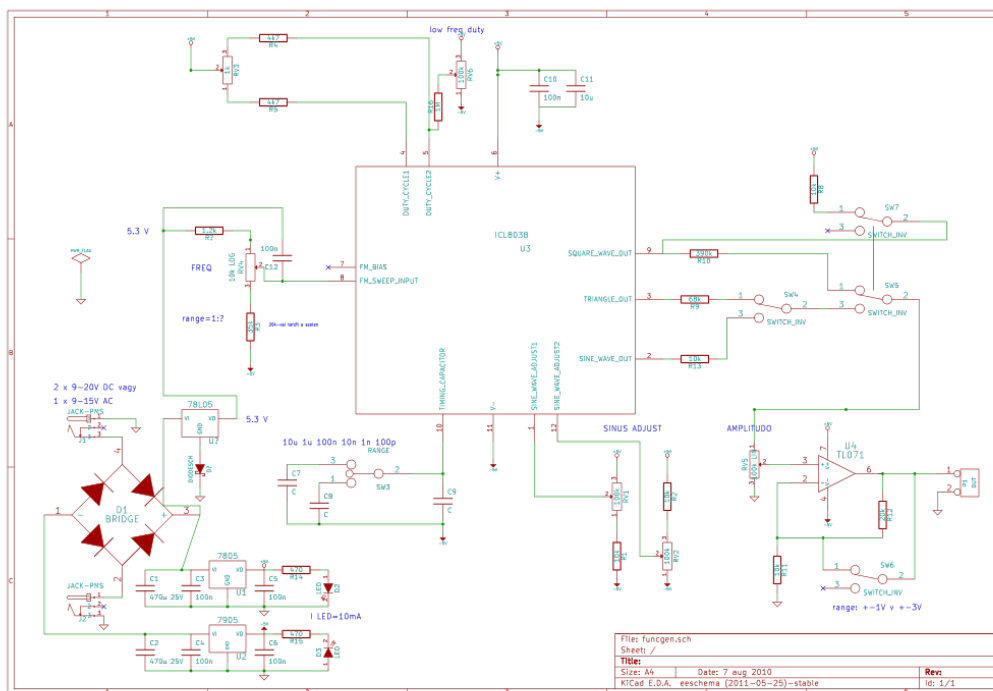

GARMIN ETREX DATA CABLE

Status: OK

It is used for connecting Garmin eTrex to the serial port.

connections:

DB9 pin	garmin pin
3 (TxD)	2 (In)
2 (RxD)	3 (Out)
5 (GND)	4 (GND)

10.1 Images




10.2 Sources

original design

IR AMPLIFIER




Status: OK

11.1 Schematic

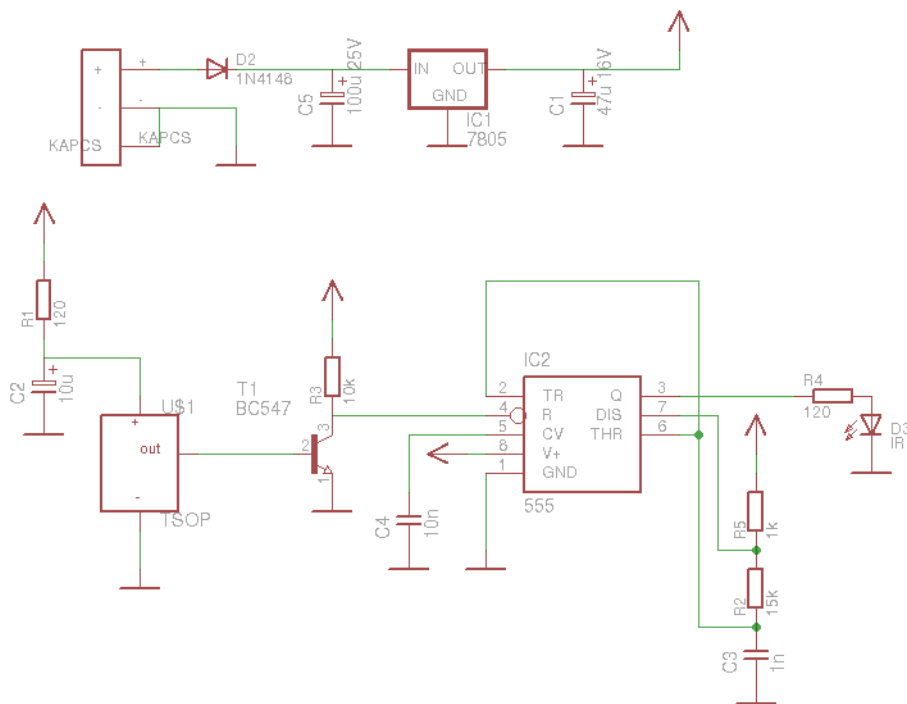

11.2 Board

Normal, bottom mirrored, wires only:

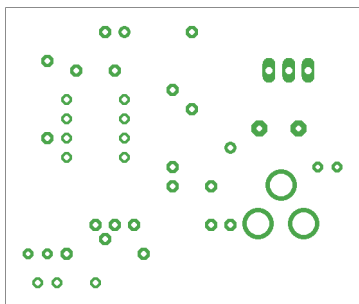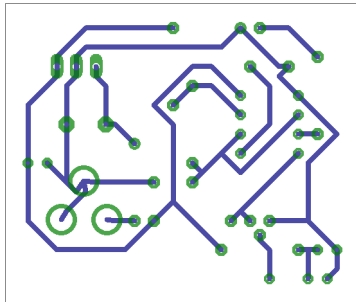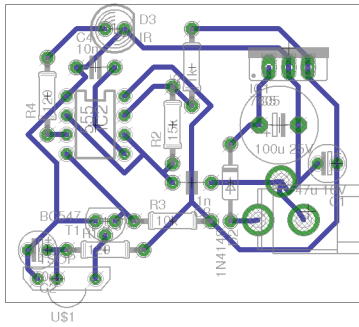


11.3 Partlist

Table 11.1:


part	value	position
C1	47u 16V	(48.26 34.29)
C2	10u	(10.16 22.86)
C3	1n	(29.21 31.75)
C4	10n	(16.51 46.99)
C5	100u 25V	(40.64 39.37)
D2	1N4148	(34.29 31.75)
D3	IR	(19.05 52.07)
IC1	7805	(41.91 49.53)
IC2	555	(16.51 39.37)
R1	120	(17.78 22.86)
R2	15k	(26.67 39.37)
R3	10k	(26.67 26.67)
R4	120	(10.16 43.18)
R5	1k	(29.21 46.99)
T1	BC547	(17.78 26.67)
U\$1	TSOP	(11.43 19.05)
U\$2	DC ALJ	(44.45 27.94)

11.4 3D view


11.4.1 Front

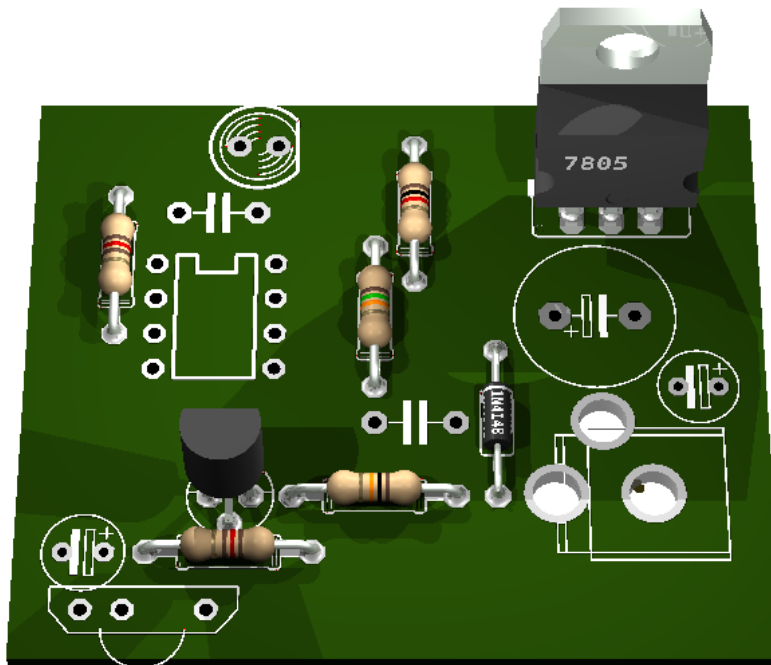


11.4.2 Right side

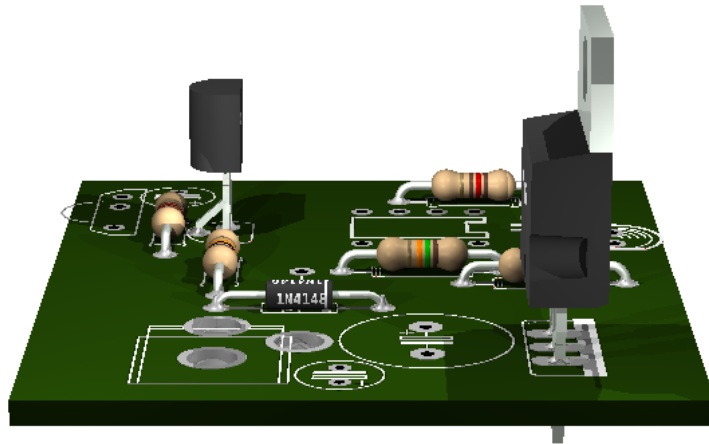

11.4.3 Left side

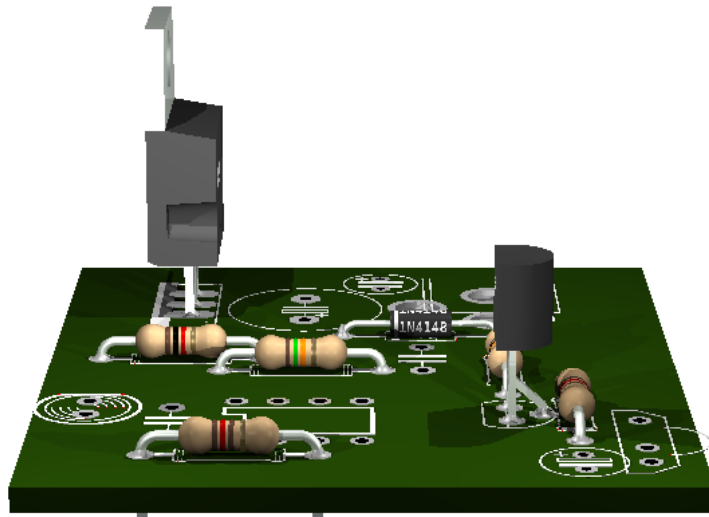

11.4.4 Bottom

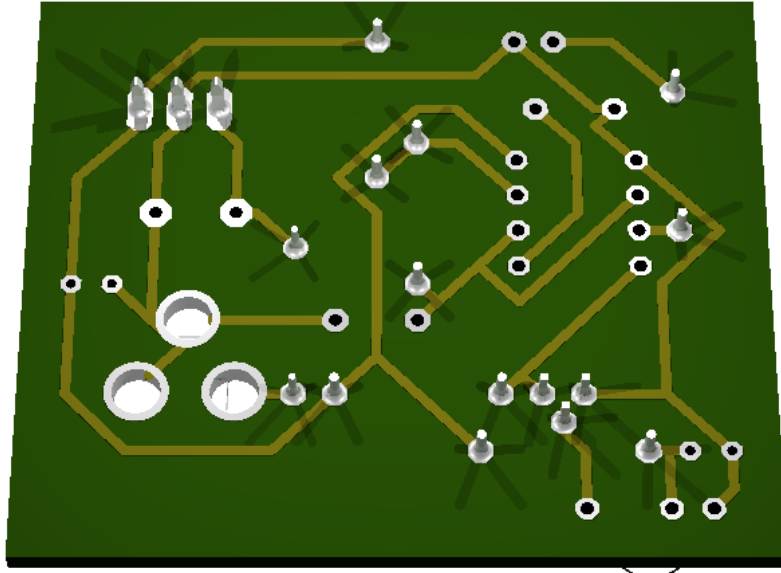

IRDA PORT

Status: OK

12.1 Schematic

source: <http://www.infrarotport.de/ir-modul.HTML>


12.2 Board

source: <http://www.infrarotport.de/platine.HTML>


LCD MODULE

Status: OK

13.1 Schematic

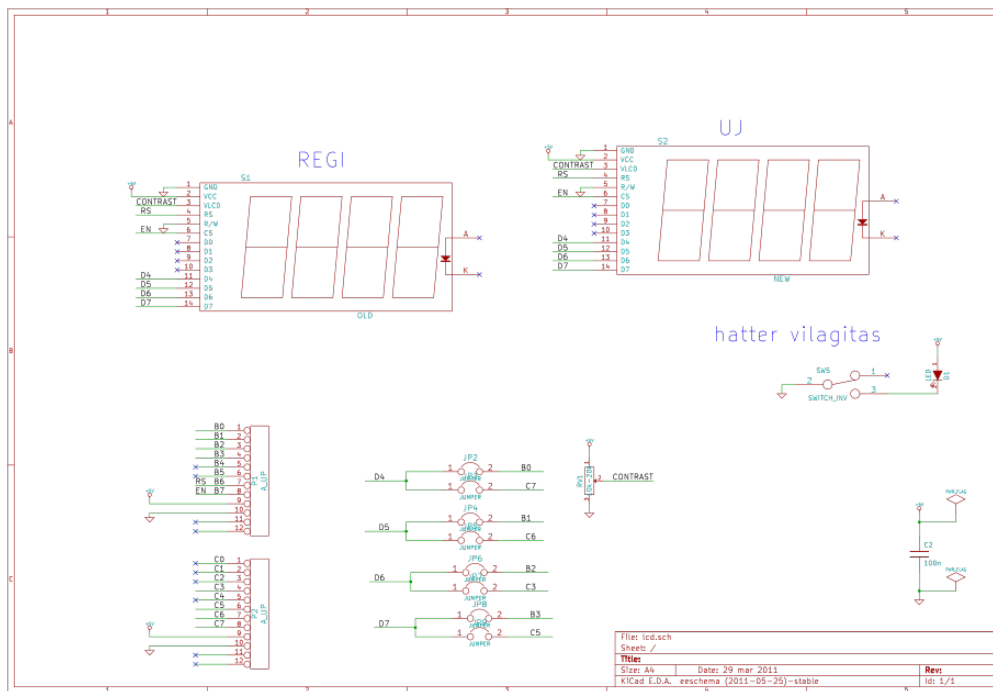


13.2 Board

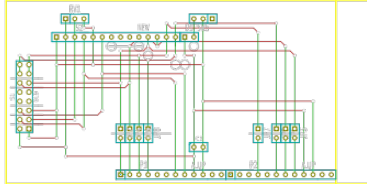

LIGHTNING DETECTOR

Status: OK

14.1 Schematic

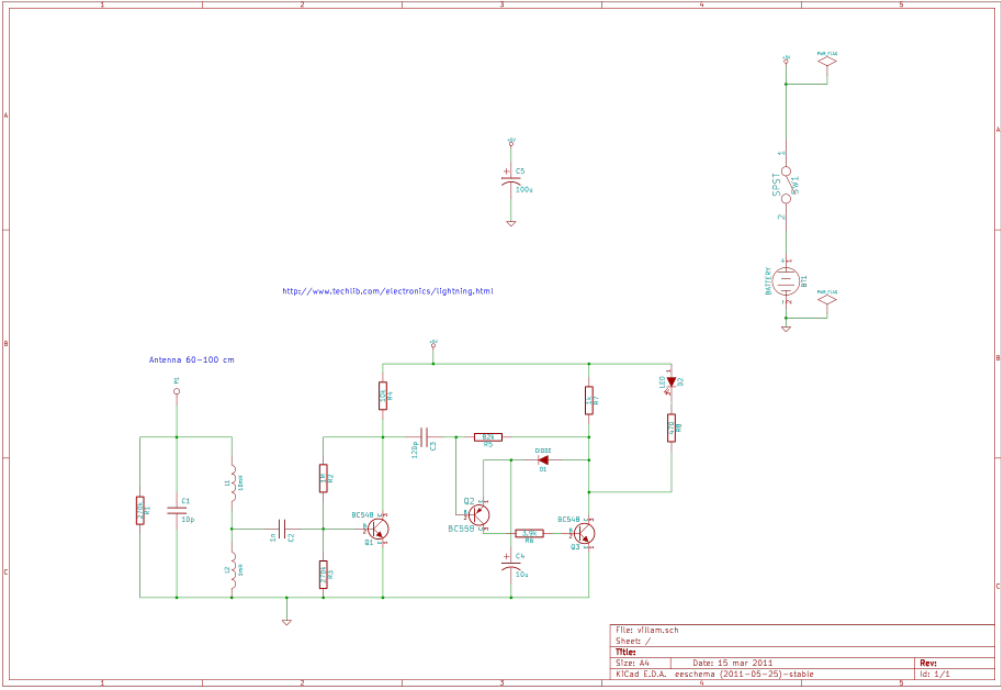


14.2 Sources

based on: <http://www.techlib.com/electronics/lightning.html>

LIRC SERIAL RECEIVER




Status: OK

15.1 Schematic

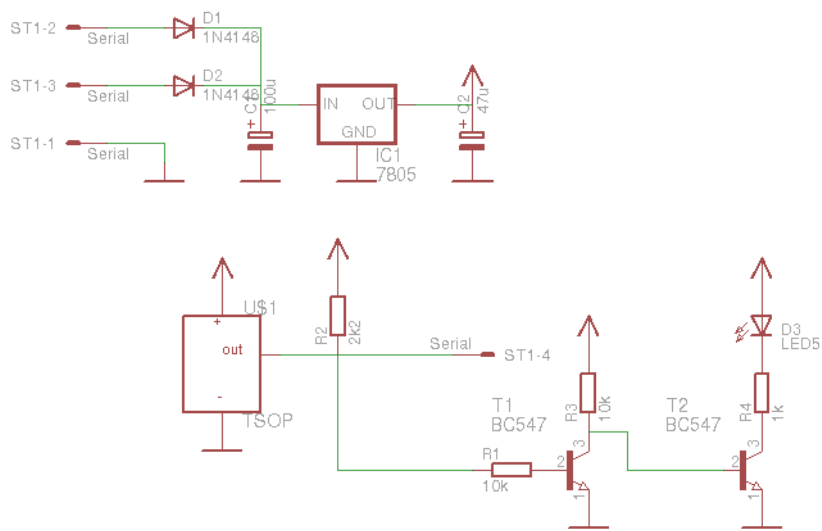

15.2 Board

Normal, bottom mirrored, wires only:

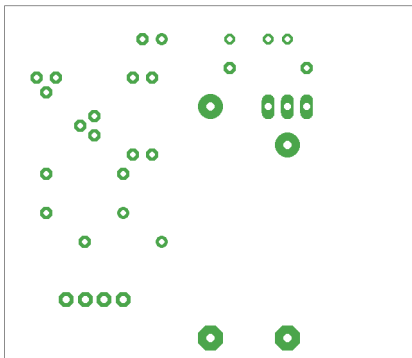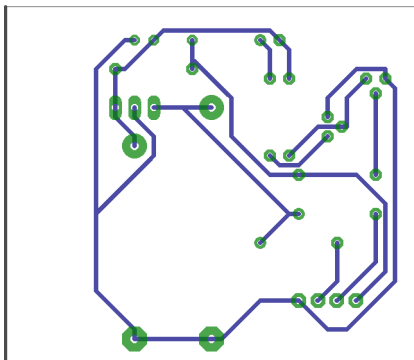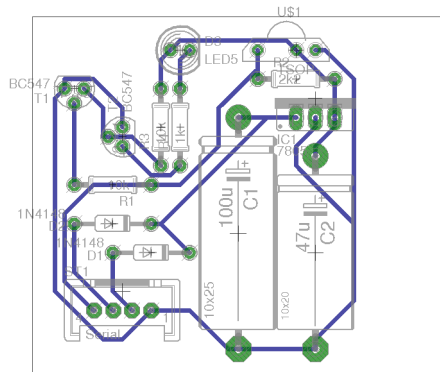

15.3 Partlist

Table 15.1:


part	value	position
C1	100u	(1.2 1.85)
C2	47u	(1.6 1.75)
D1	1N4148	(0.75 1.75)
D2	1N4148	(0.55 1.9)
D3	LED5	(0.9 2.8)
IC1	7805	(1.6 2.55)
R1	10k	(0.55 2.1)
R2	2k2	(1.5 2.65)
R3	10k	(0.8 2.4)
R4	1k	(0.9 2.4)
ST1	Serial	(0.6 1.55)
T1	BC547	(0.35 2.6)
T2	BC547	(0.6 2.35)
U\$1	TSOP	(1.5 2.8)

15.4 3D view


15.4.1 Front




15.4.2 Right side

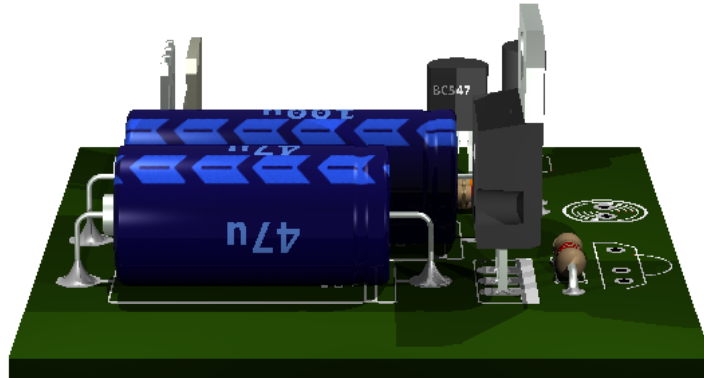

15.4.3 Left side

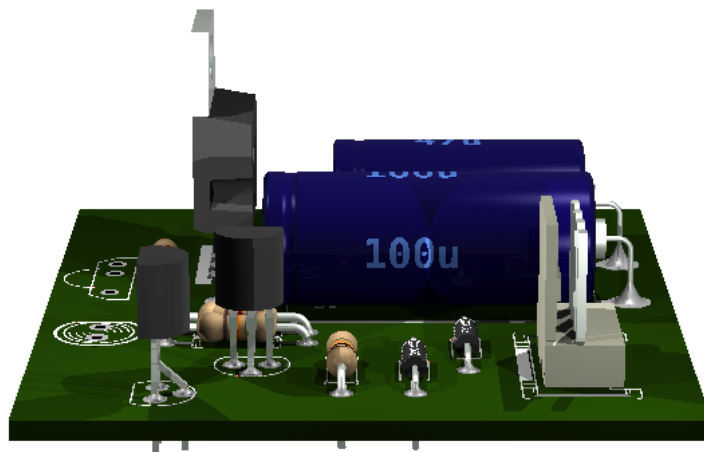

15.4.4 Bottom

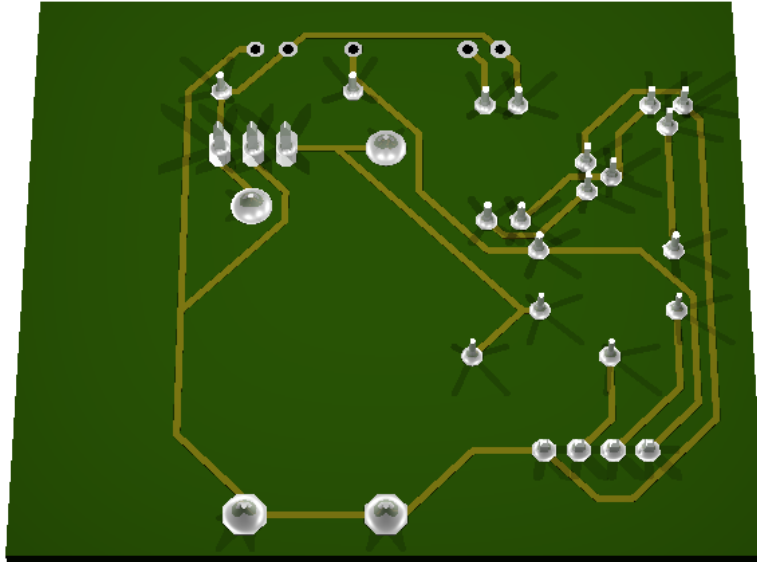

LOGIC PROBE

Status: OK

It is used for testing logic levels.

Vcc=3-15V

Source: <http://www.sentex.net/~mec1995/circ/probe2.htm>

Differences:

- R2=4M7
- R3=1k
- R4=1k
- R5=1k
- LED + 1k for Power



NOKIA ADAPTER

Status: OK

17.1 Sources

original design

GSM CABLES
<http://gsm-cables.com>

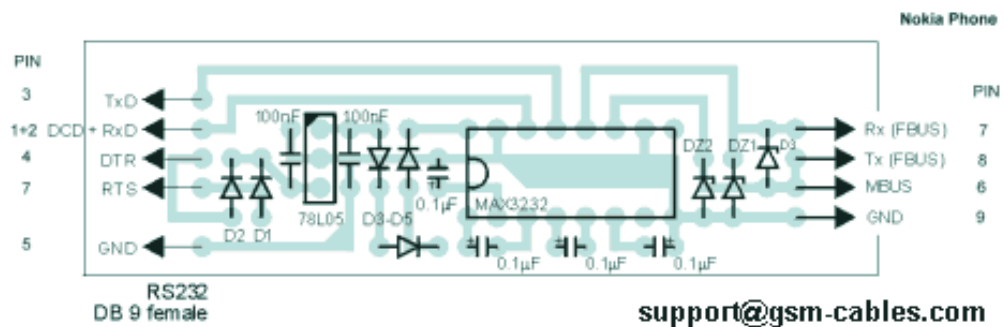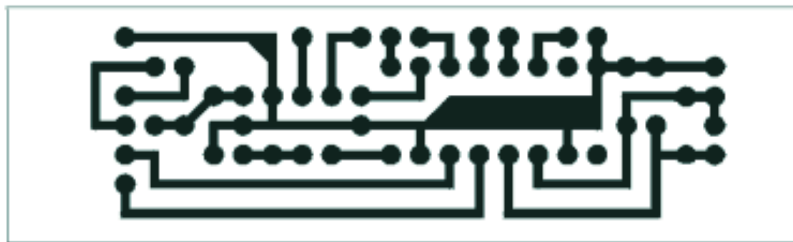


OP-AMP MODULE

Status: OK


It is used for op-amps in breadboard.

18.1 Schematic

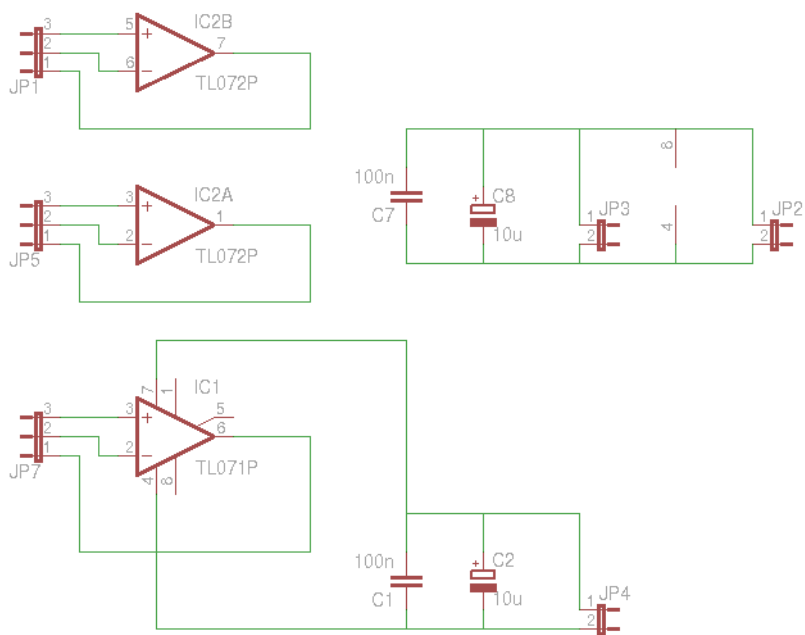


18.2 Board


top

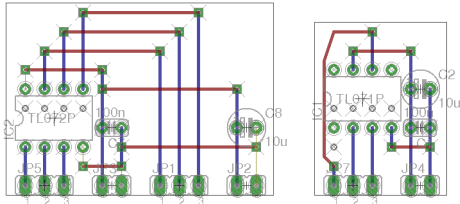


bottom mirrored

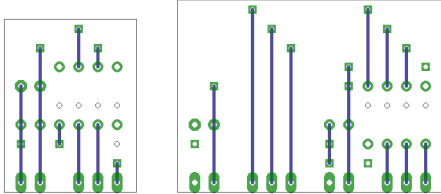

wires only

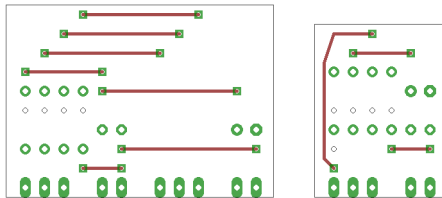

document

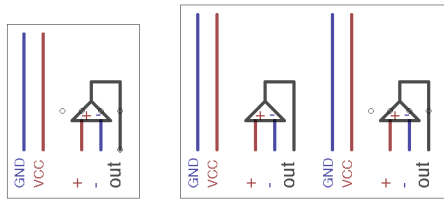


18.3 Partlist

Table 18.1:


part	value	position
C1	100n	(2.35 0.4)
C2	10u	(2.35 0.6)
C7	100n	(0.75 0.4)
C8	10u	(1.45 0.4)
IC1	TL071P	(2.05 0.55)
IC2	TL072P	(0.45 0.45)
JP1		(1.1 0.1)
JP2		(1.45 0.1)
JP3		(0.75 0.1)
JP4		(2.35 0.1)
JP5		(0.4 0.1)
JP7		(2 0.1)

18.4 3D view


18.4.1 Front

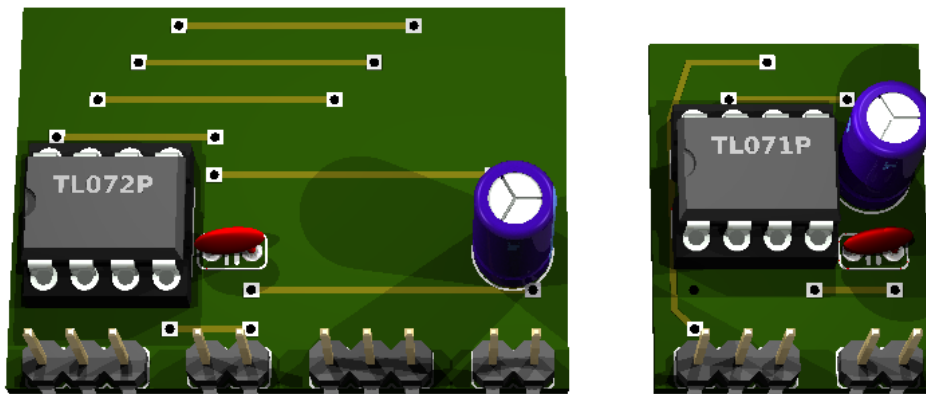


18.4.2 Right side

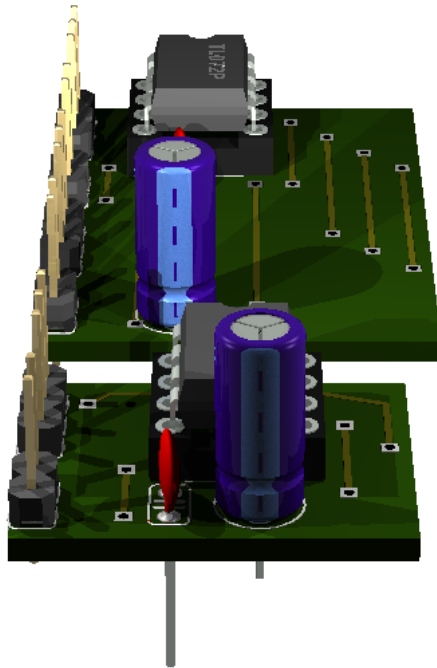

18.4.3 Left side

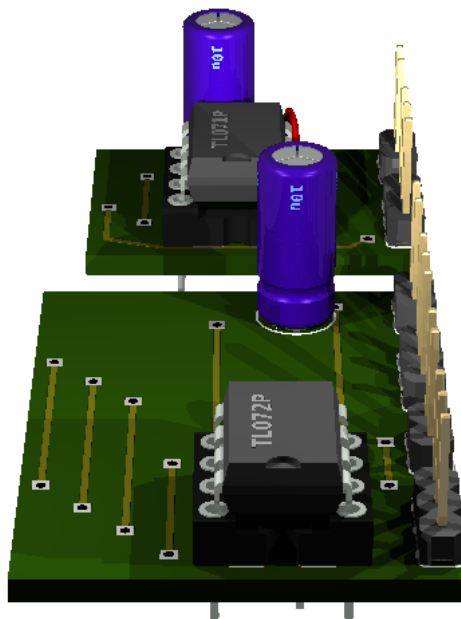

18.4.4 Bottom

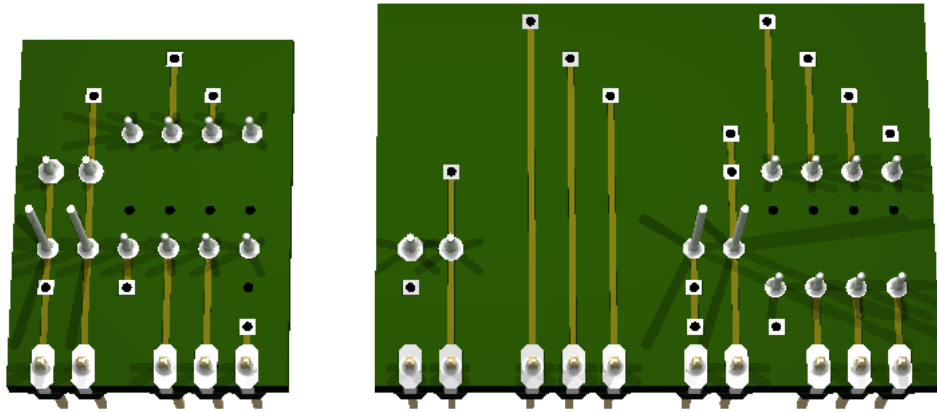


OUTLET TESTER

Status: ??


This device is used to verify that an 230V AC wall outlet is wired properly.


19.1 Schematic

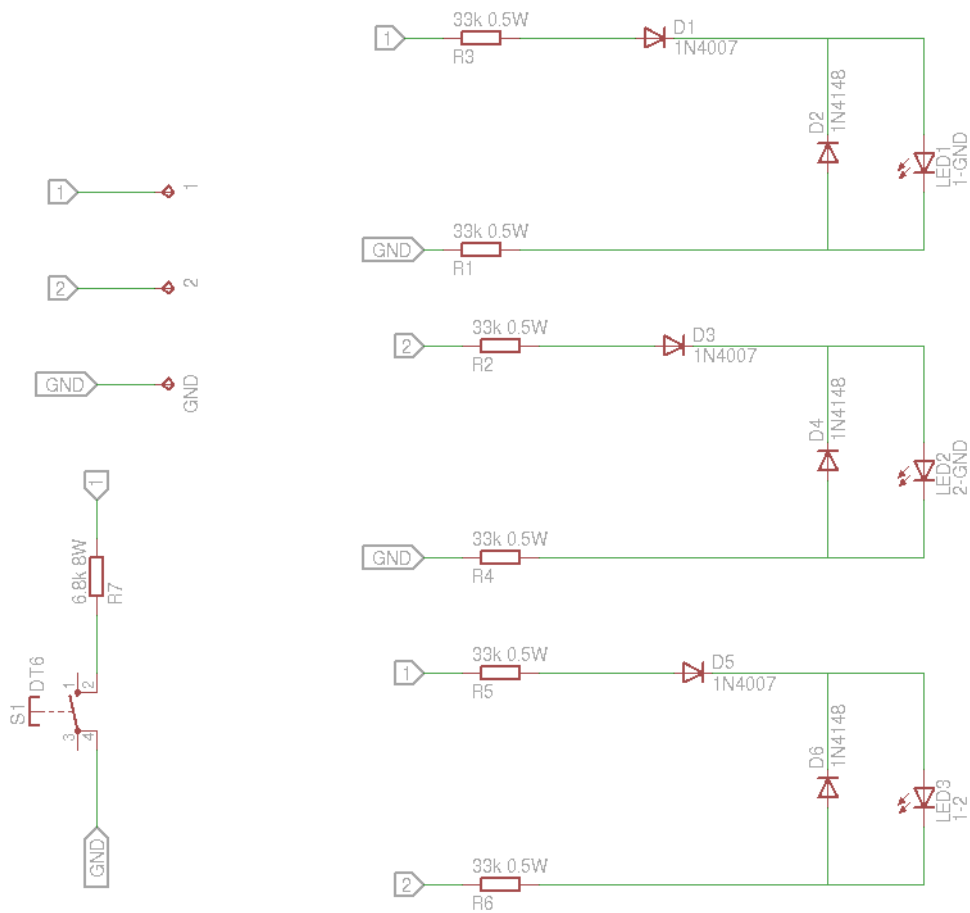

19.2 Board

Normal, bottom mirrored, wires only:

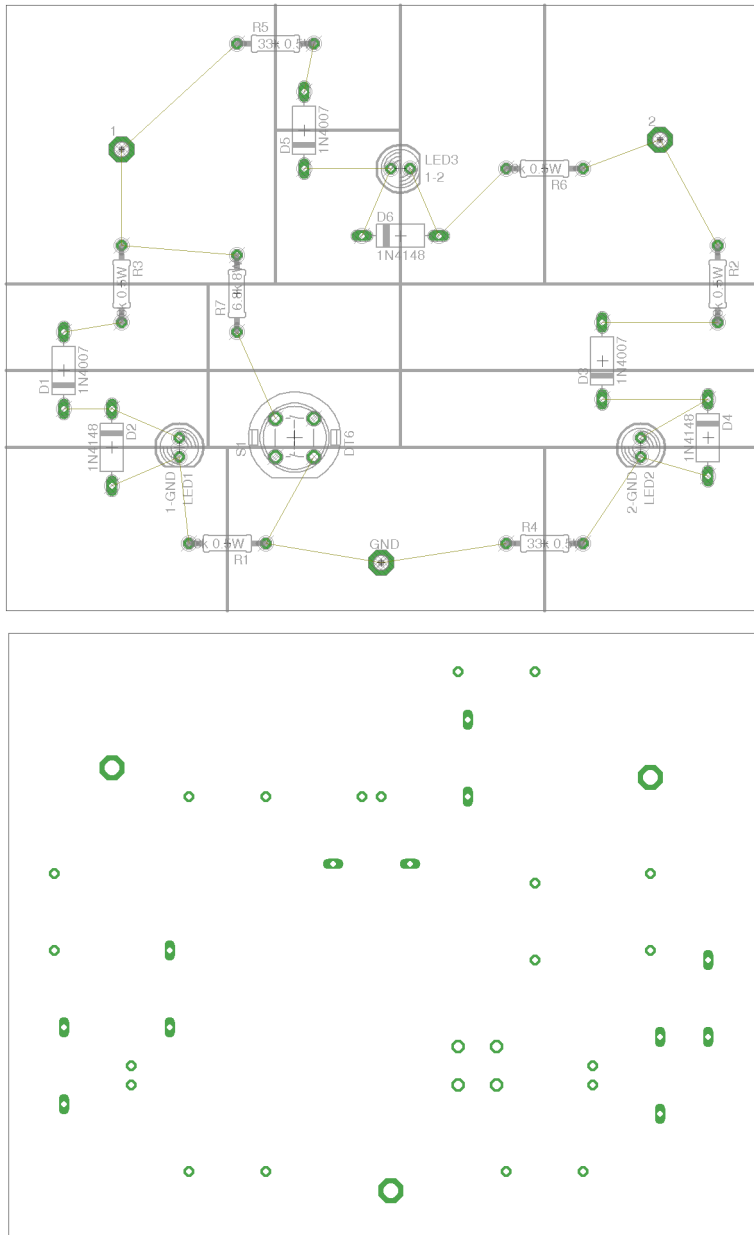

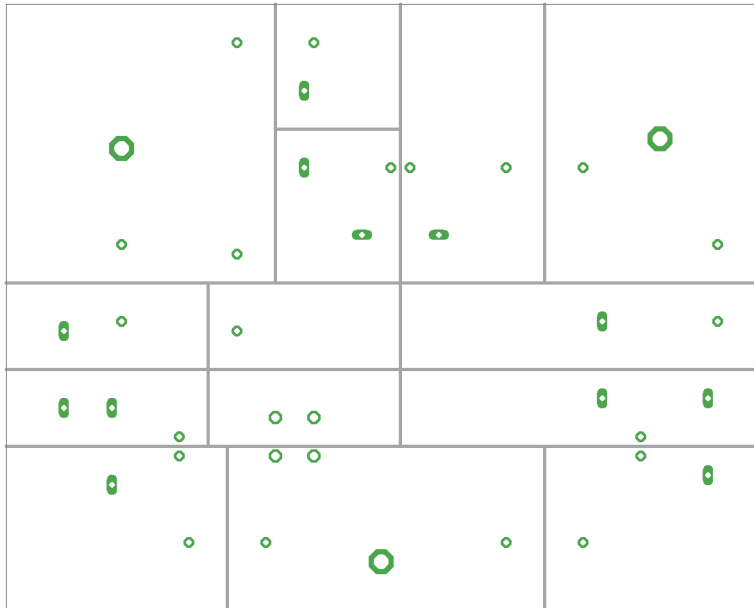


19.3 Partlist

Table 19.1:


part	value	position
1	TPPAD1-20	(0.6 2.4)
2	TPPAD1-20	(3.4 2.45)
D1	1N4007	(0.3 1.25)
D2	1N4148	(0.55 0.85)
D3	1N4007	(3.1 1.3)
D4	1N4148	(3.65 0.9)
D5	1N4007	(1.55 2.5)
D6	1N4148	(2.05 1.95)
GND	TPPAD1-20	(1.95 0.25)
LED1	1-GND	(0.9 0.85)
LED2	2-GND	(3.3 0.85)
LED3	1-2	(2.05 2.3)
R1	33k 0.5W	(1.15 0.35)
R2	33k 0.5W	(3.7 1.7)
R3	33k 0.5W	(0.6 1.7)
R4	33k 0.5W	(2.8 0.35)
R5	33k 0.5W	(1.4 2.95)
R6	33k 0.5W	(2.8 2.3)
R7	6.8k 8W	(1.2 1.65)
S1	DT6	(1.5 0.9)

19.4 3D view


19.4.1 Front

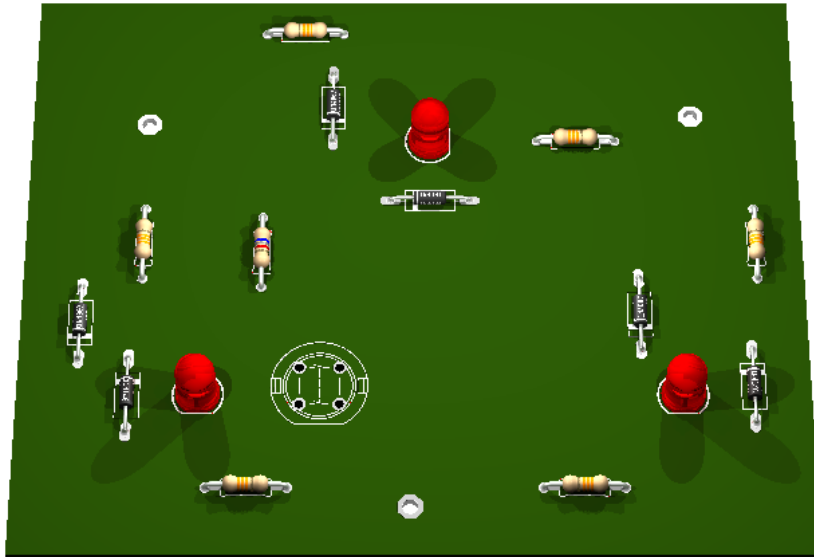


19.4.2 Right side

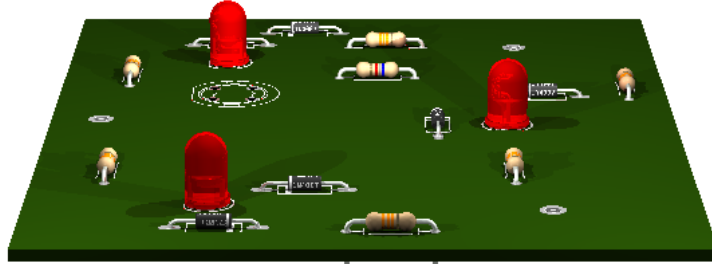

19.4.3 Left side

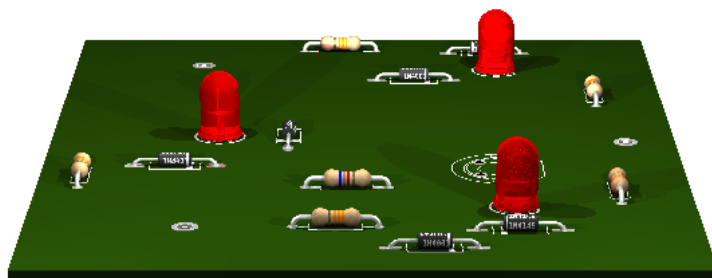

19.4.4 Bottom

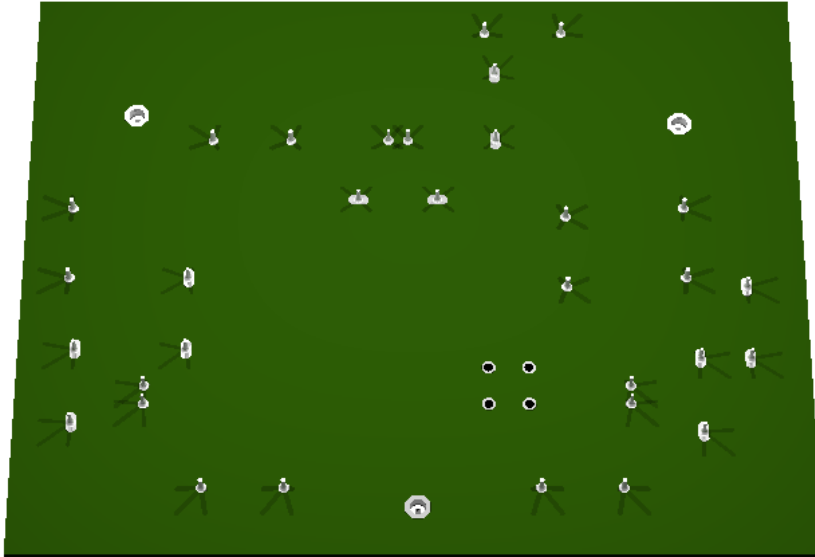

19.5 Sources


http://en.wikipedia.org/wiki/Receptacle_tester


PARALLEL PORT MONITOR

Status: OK





It is used for monitoring the parallel port signals.

20.1 Images

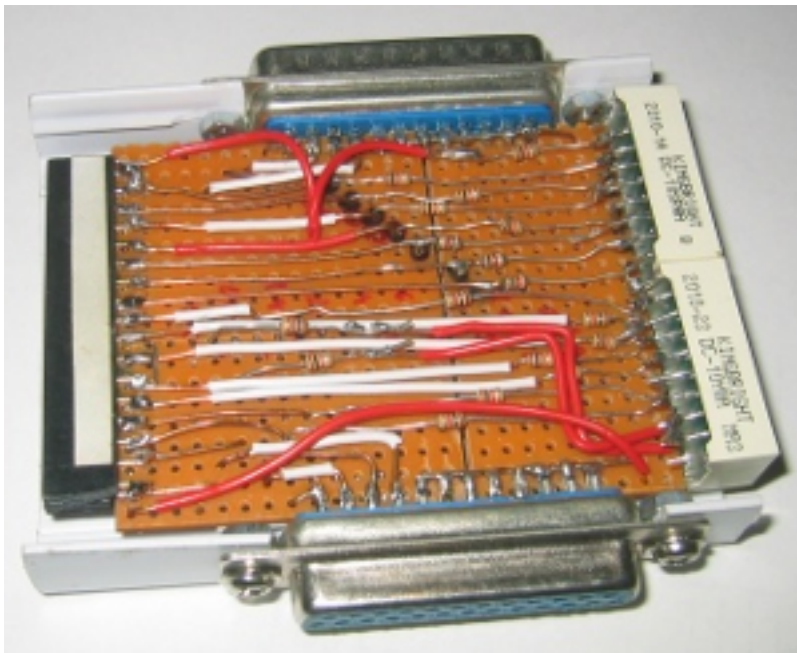

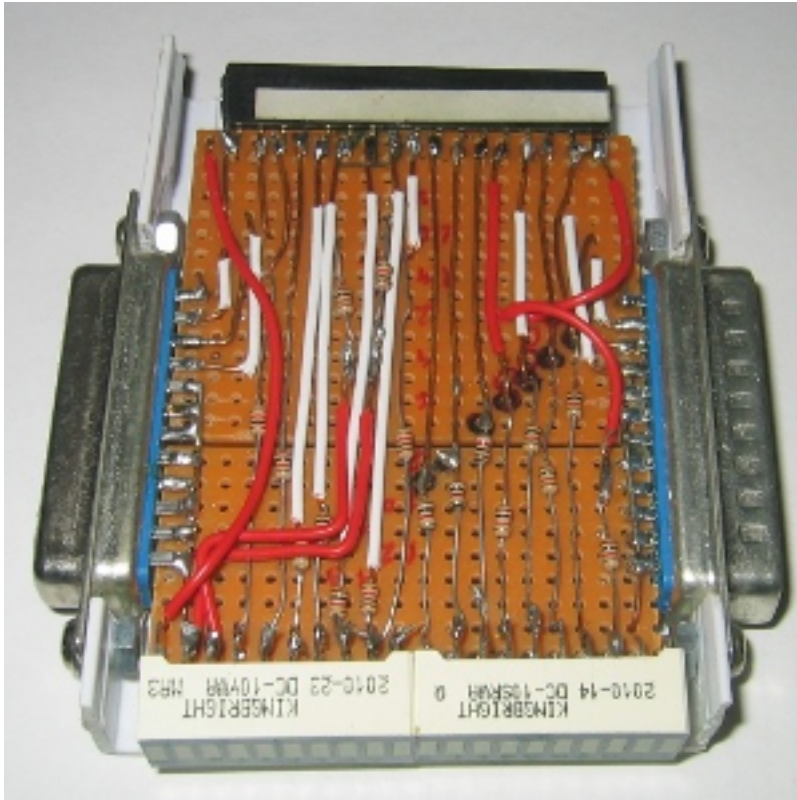



20.2 Schematic

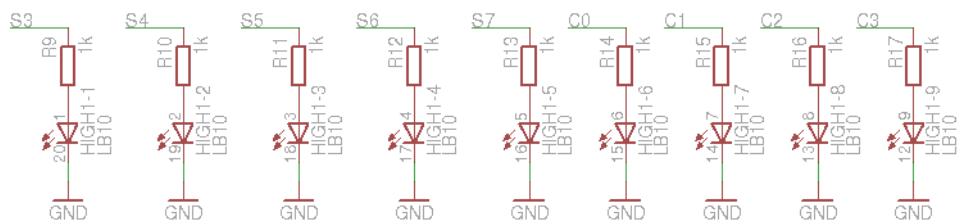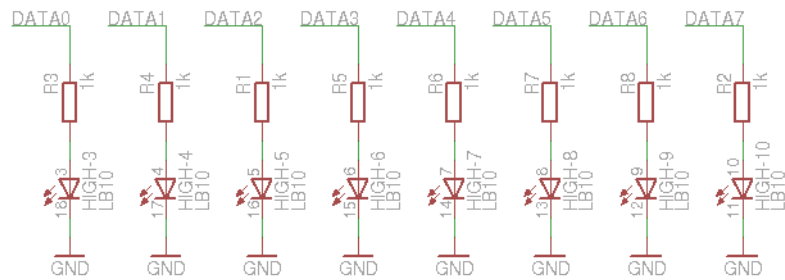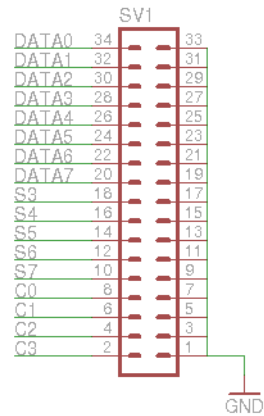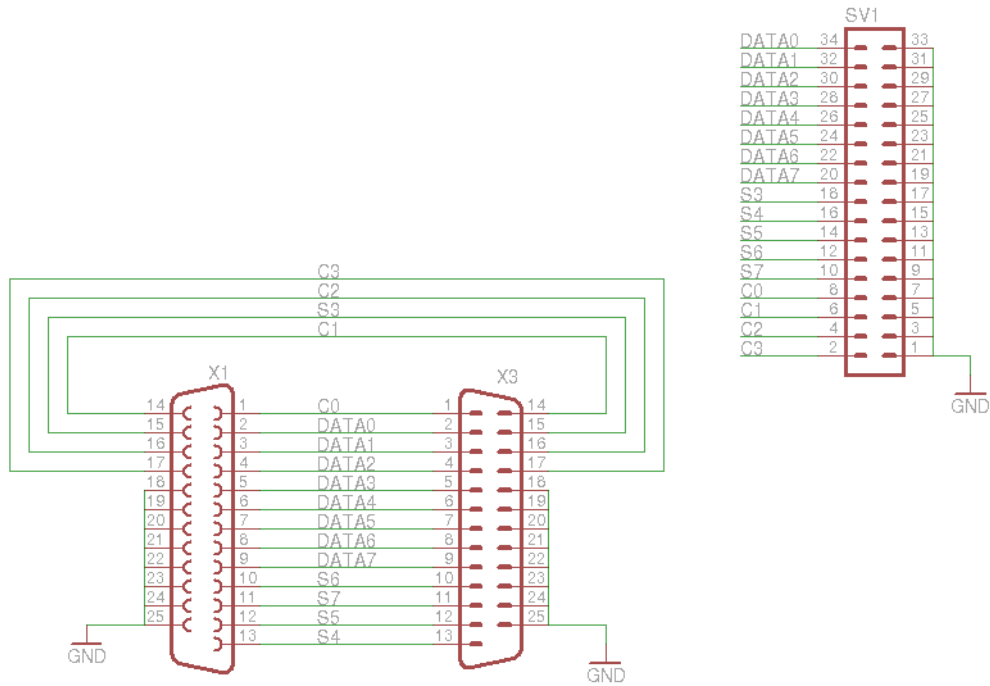

20.3 Board

Normal, bottom mirrored, wires only:

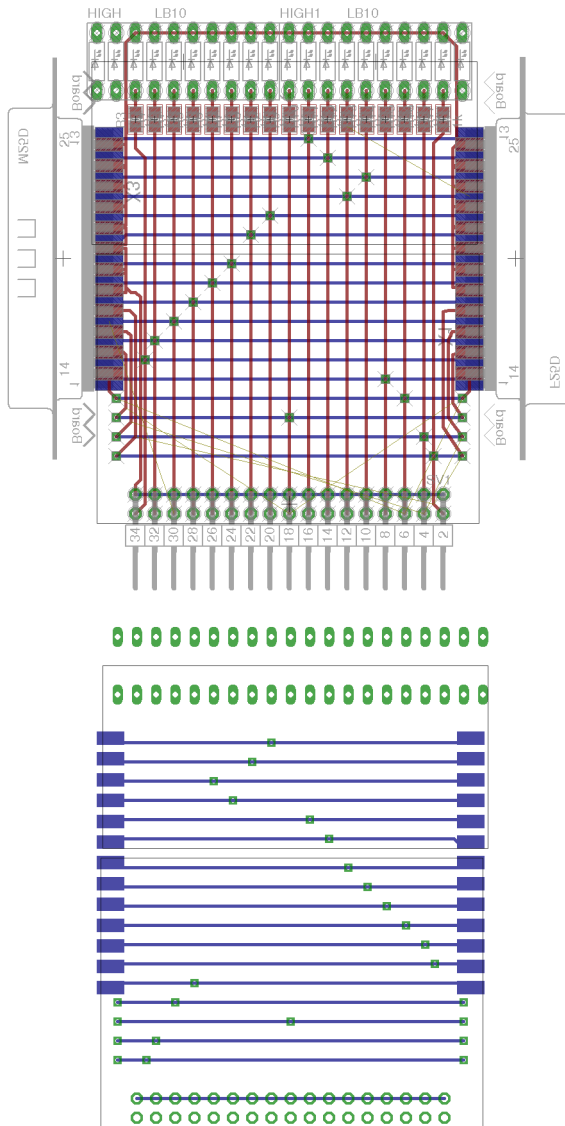

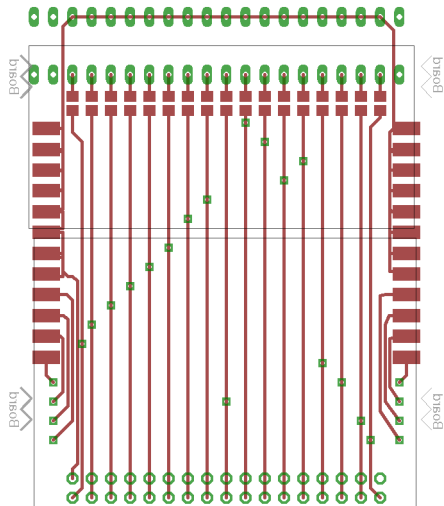


20.4 Partlist

Table 20.1:


part	value	position
HIGH	LB10	(0.45 2.55)
HIGH1	LB10	(1.45 2.55)
R1	1k	(0.4 2.25)
R2	1k	(0.9 2.25)
R3	1k	(0.2 2.25)
R4	1k	(0.3 2.25)
R5	1k	(0.5 2.25)
R6	1k	(0.6 2.25)
R7	1k	(0.7 2.25)
R8	1k	(0.8 2.25)
R9	1k	(1 2.25)
R10	1k	(1.1 2.25)
R11	1k	(1.2 2.25)
R12	1k	(1.3 2.25)
R13	1k	(1.4 2.25)
R14	1k	(1.5 2.25)
R15	1k	(1.6 2.25)
R16	1k	(1.7 2.25)
R17	1k	(1.8 2.25)
SV1		(1 0.25)
X1		(2.175 1.525)
X3		(-0.175 1.525)

20.5 3D view


20.5.1 Front

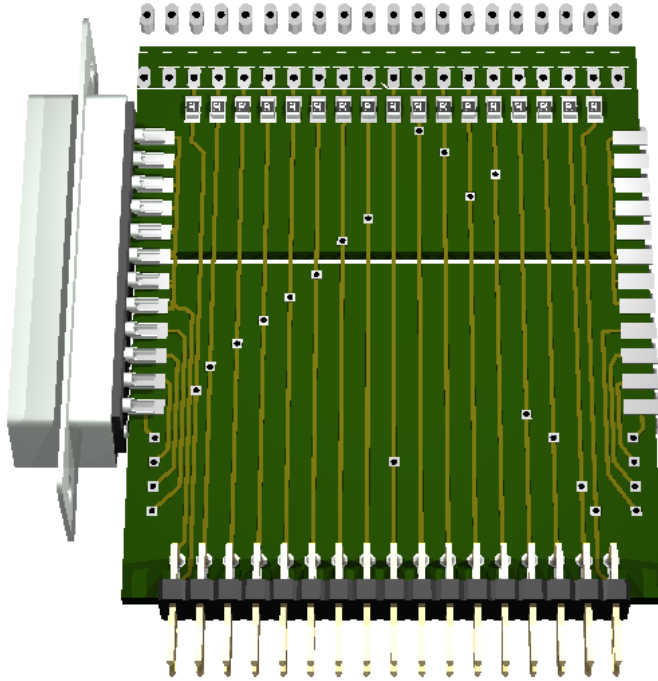


20.5.2 Right side

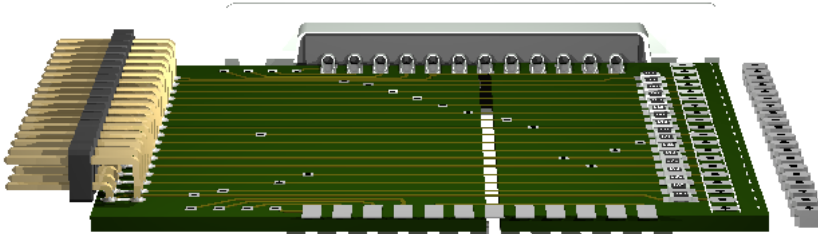

20.5.3 Left side

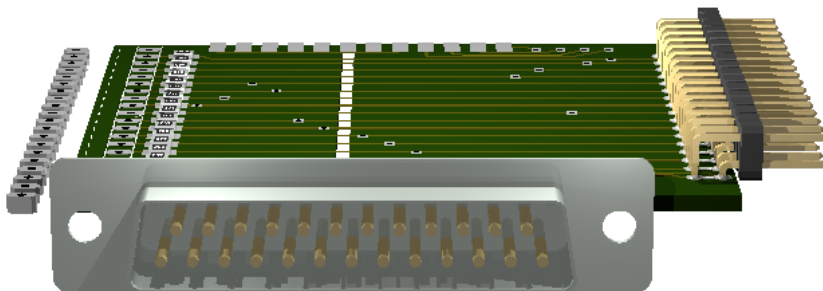

20.5.4 Bottom

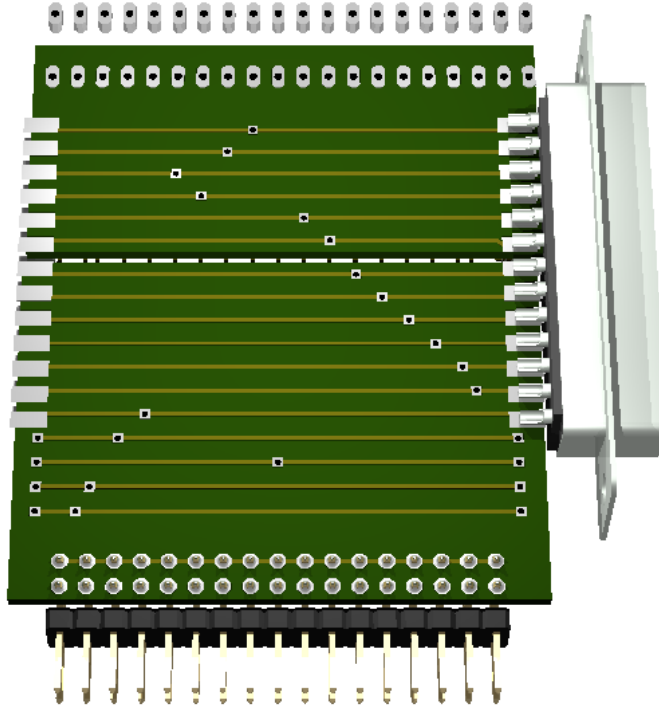

20.6 Sources


original idea

PIC ICSP PROGRAMMER


Status: OK

It is used for programming PIC using the parallel port.

21.1 Schematic

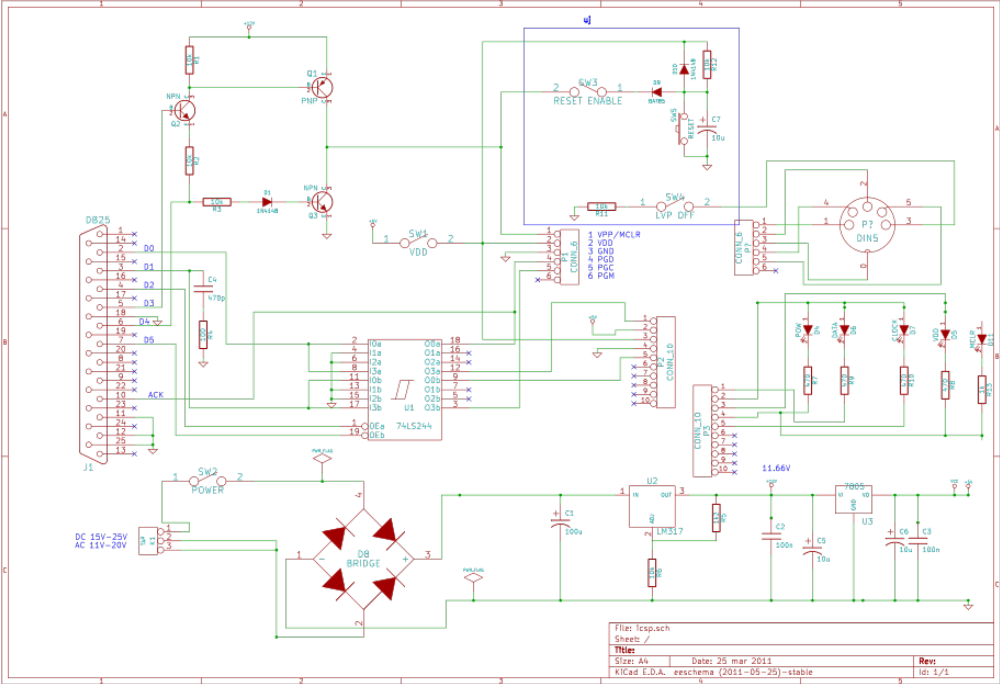

21.2 Board

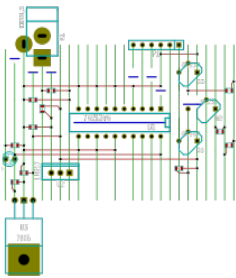

21.3 Sources

original design: <http://www.best-microcontroller-projects.com/pic-programmer-circuit.html>

which is based on: http://www.microchip.com/stellent/idcplg?IdcService=SS_GET_PAGE&nodeId=1824&appnote=en011060

PONG

Status: OK


Arduino based pong console

Pong firmware: <https://github.com/ponty/arduino-pong>

program config:




```
const int pin_wheel1 = 4; // analog
const int pin_wheel2 = 5; // analog
const int pin_button1 = 4;
const int pin_audio = 10;
```

22.1 Schematic

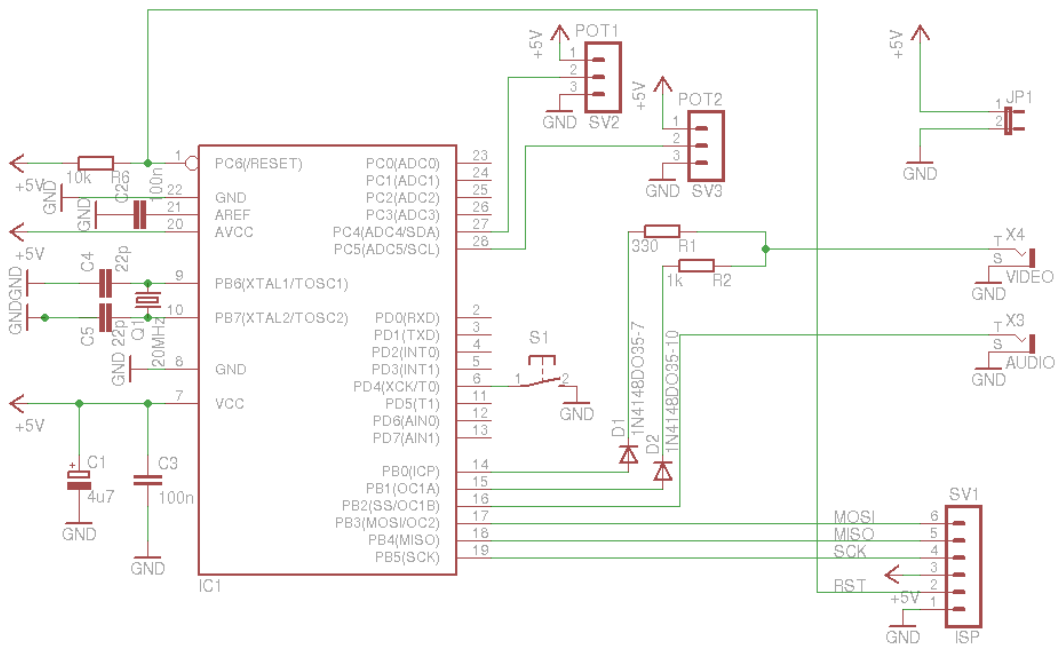

22.2 Board

Normal, bottom mirrored, wires only:

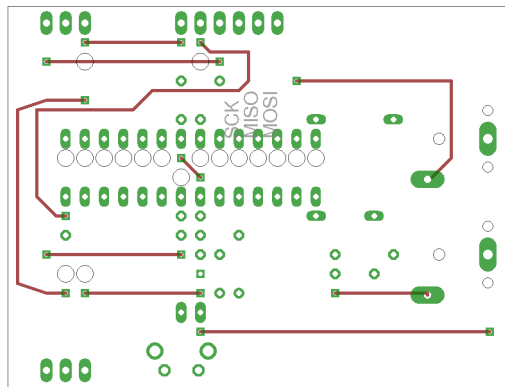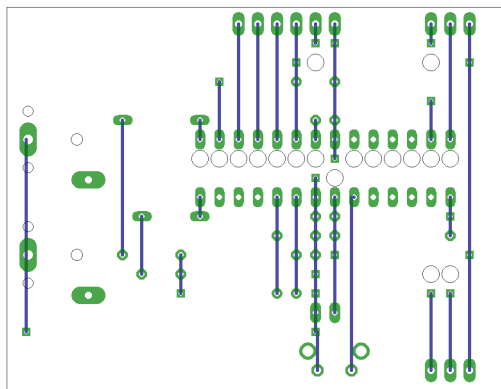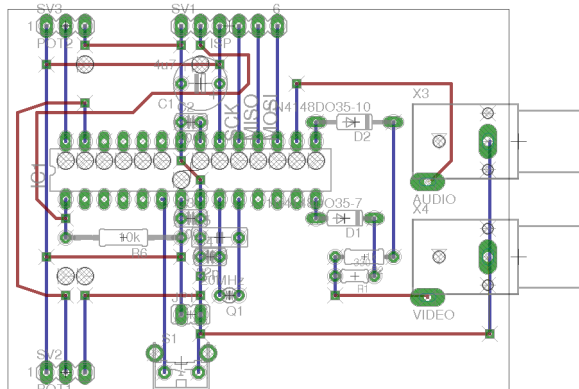


22.3 Partlist

Table 22.1:


part	value	position
C1	4u7	(1.1 1.7)
C2	100n	(1.05 1.5)
C3	100n	(1.05 1)
C4	22p	(1.15 0.8)
C5	22p	(1.2 0.9)
D1	1N4148DO35-7	(1.85 1)
D2	1N4148DO35-10	(1.9 1.5)
IC1		(1.05 1.25)
JP1		(1.05 0.5)
Q1	20MHz	(1.25 0.6)
R1	330	(1.9 0.7)
R2	1k	(1.95 0.8)
R6	10k	(0.7 0.9)
S1		(1 0.25)
SV1	ISP	(1.25 2)
SV2	POT1	(0.4 0.2)
SV3	POT2	(0.4 2)
X3	AUDIO	(2.75 1.4)
X4	VIDEO	(2.75 0.8)

22.4 3D view


22.4.1 Front

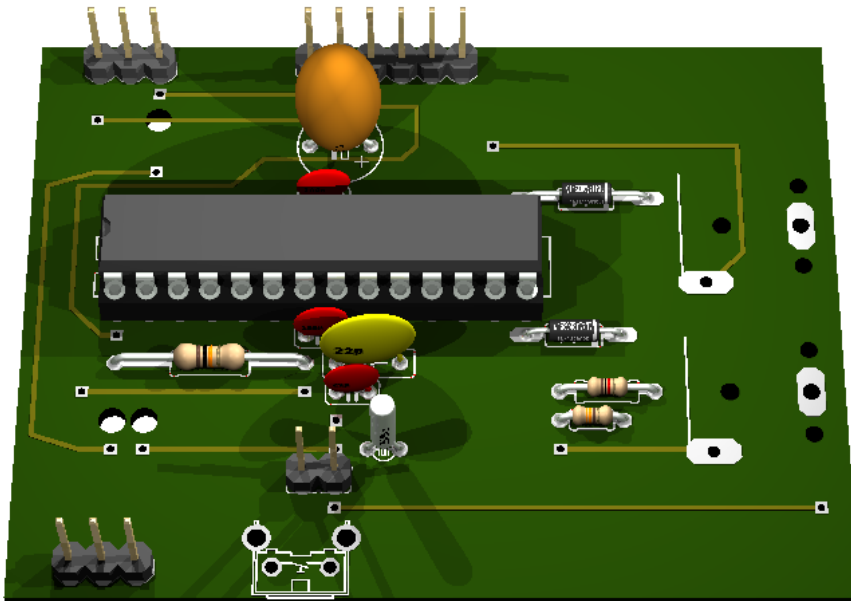


22.4.2 Right side

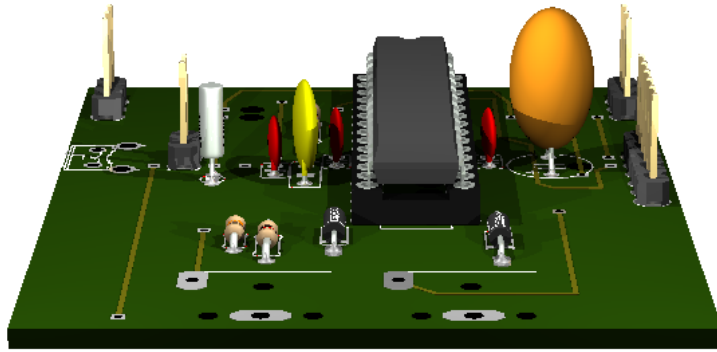

22.4.3 Left side

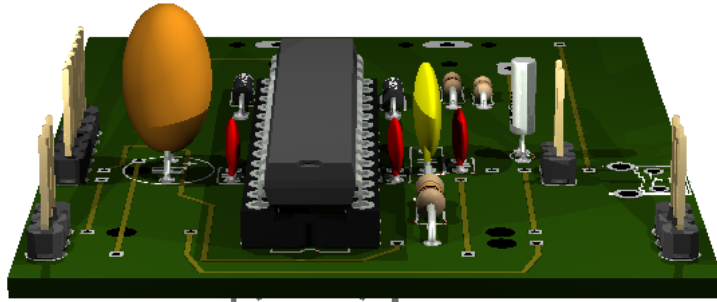

22.4.4 Bottom

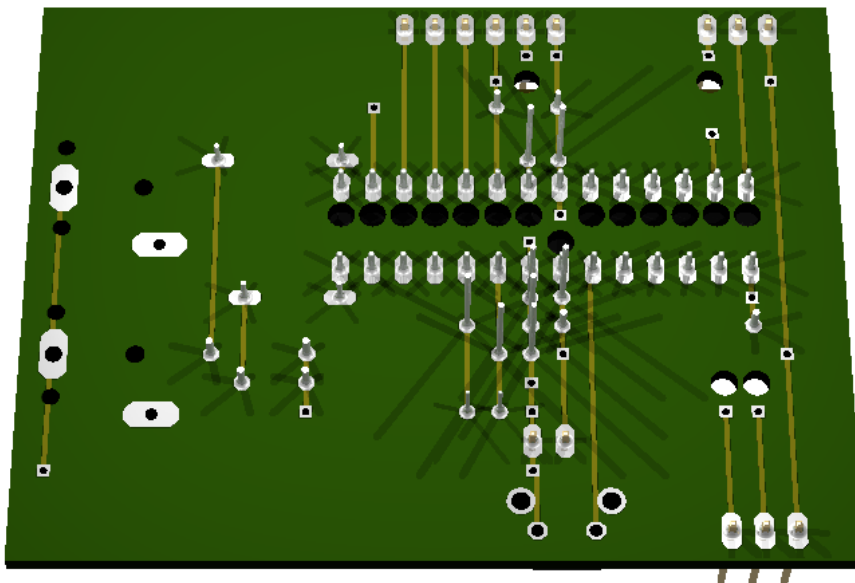

22.5 Sources


similar projects:

- <http://www.instructables.com/id/Ardu-pong-the-Arduino-based-pong-console/>
- <http://www.instructables.com/id/2-player-Pong-using-Arduino/>
- <http://blog.makezine.com/2007/08/22/arduino-pong/>


POWER SUPPLY

Status: OK
LM317 based power supply.

23.1 Schematic

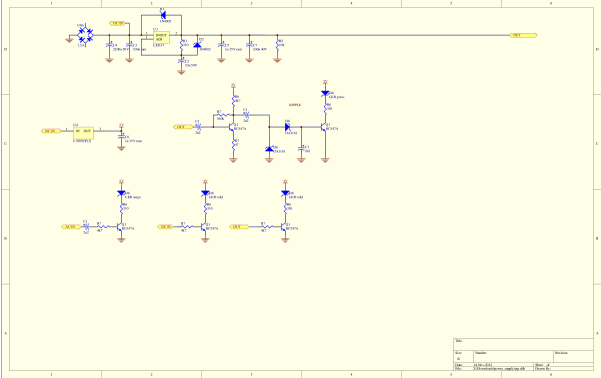


23.2 Board

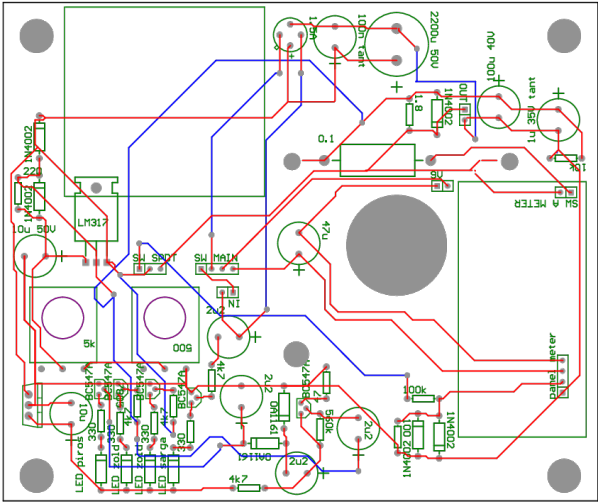

PREAMPLIFIER


Status:

24.1 Schematic

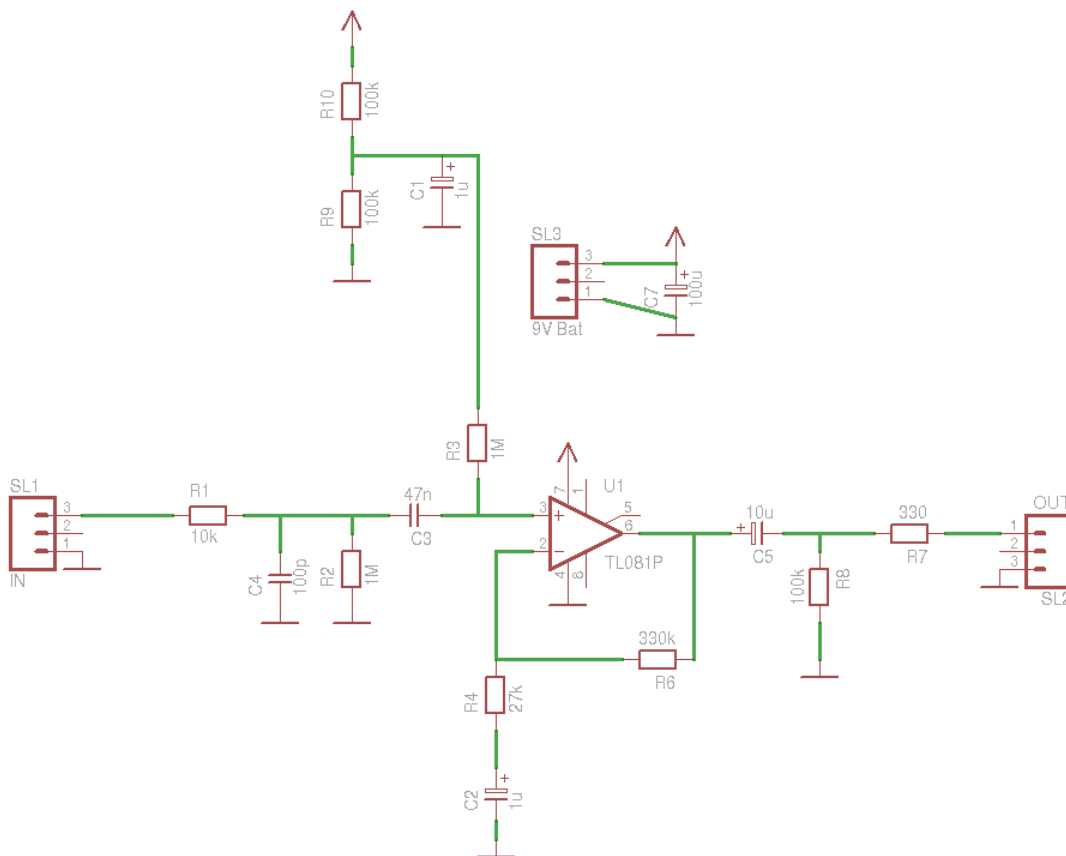

24.2 Board

Normal, bottom mirrored, wires only:

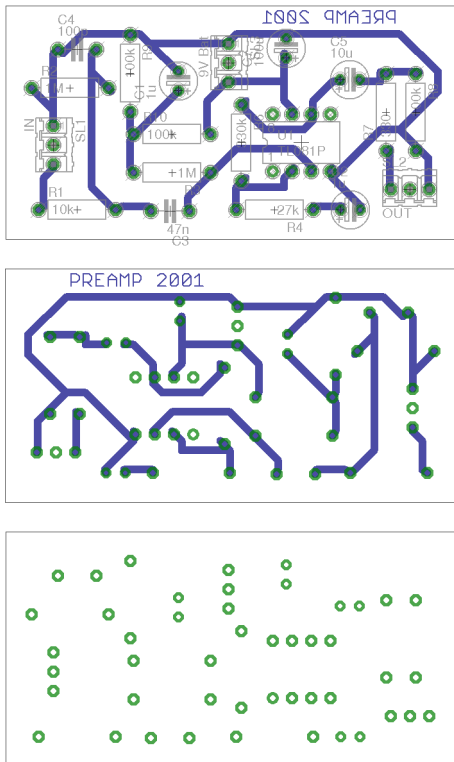


24.3 Partlist

Table 24.1:


part	value	position
C1	1u	(20.28 19.21)
C2	1u	(41.69 3.37)
C3	47n	(19.21 3.21)
C4	100p	(6.97 24.58)
C5	10u	(41.66 20.61)
C7	100u	(34.5 23.53)
R1	10k	(6.97 3.42)
R2	1M	(5.97 19.5)
R3	1M	(19.48 8.29)
R4	27k	(32.99 3.37)
R6	330k	(28.64 12.26)
R7	330	(47.72 16.31)
R8	100k	(51.64 16.31)
R9	100k	(13.93 21.48)
R10	100k	(19.48 13.37)
SL1	IN	(3.81 11.96)
SL2	OUT	(50.82 6.12)
SL3	9V Bat	(26.88 22.8)
U1	TL081P	(36.53 12.26)

24.4 3D view


24.4.1 Front

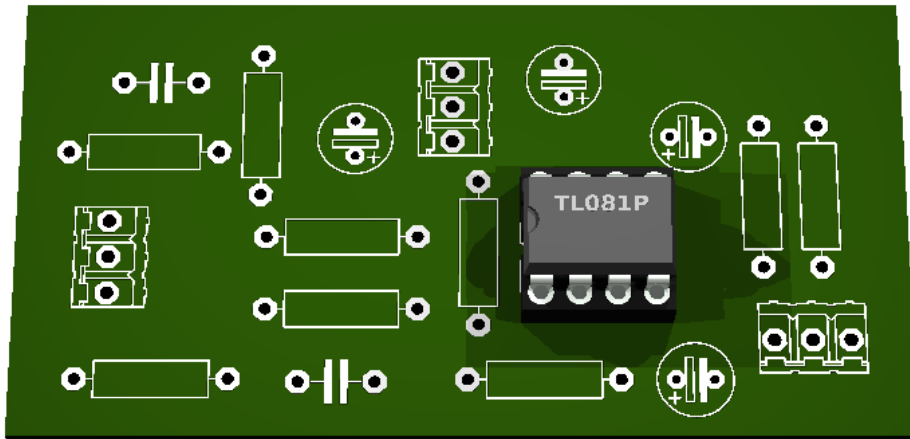


24.4.2 Right side

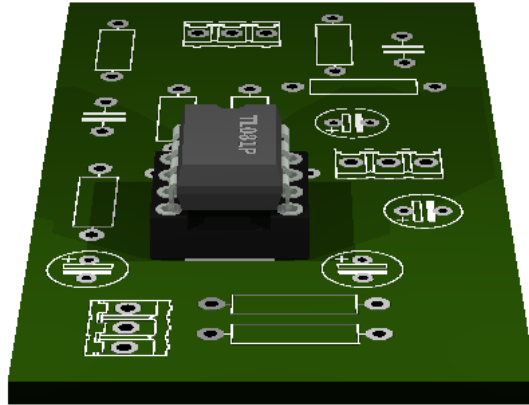

24.4.3 Left side

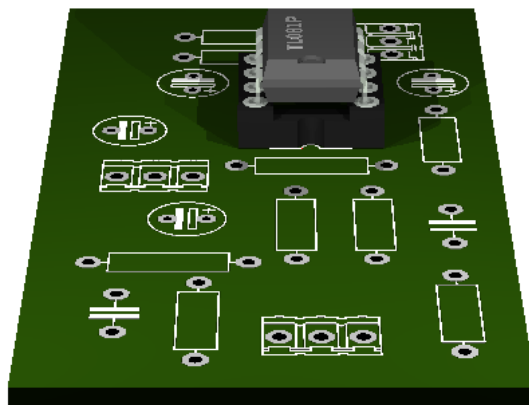

24.4.4 Bottom

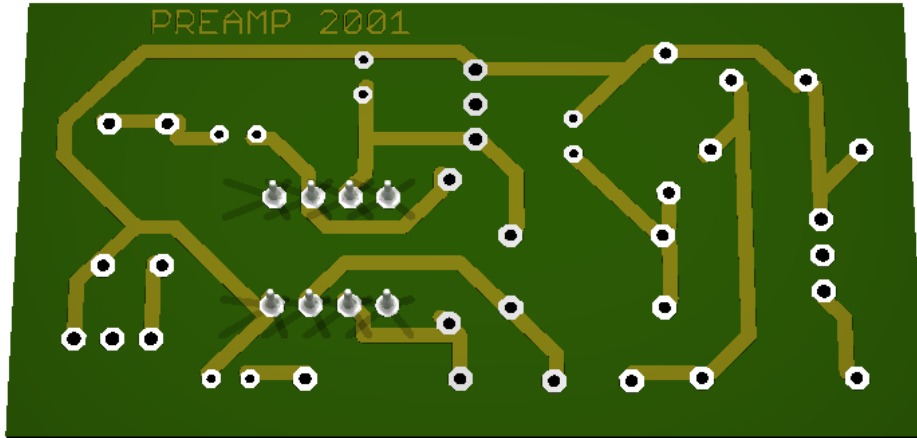

24.5 Sources


original design

BOB BLICK

CALCULATION SHEET

BY _____ DATE 10/31/95 SUBJECT Guitar Preamp SHEET NO. _____ OF _____


CHKD _____ DATE _____ JOB NO. _____


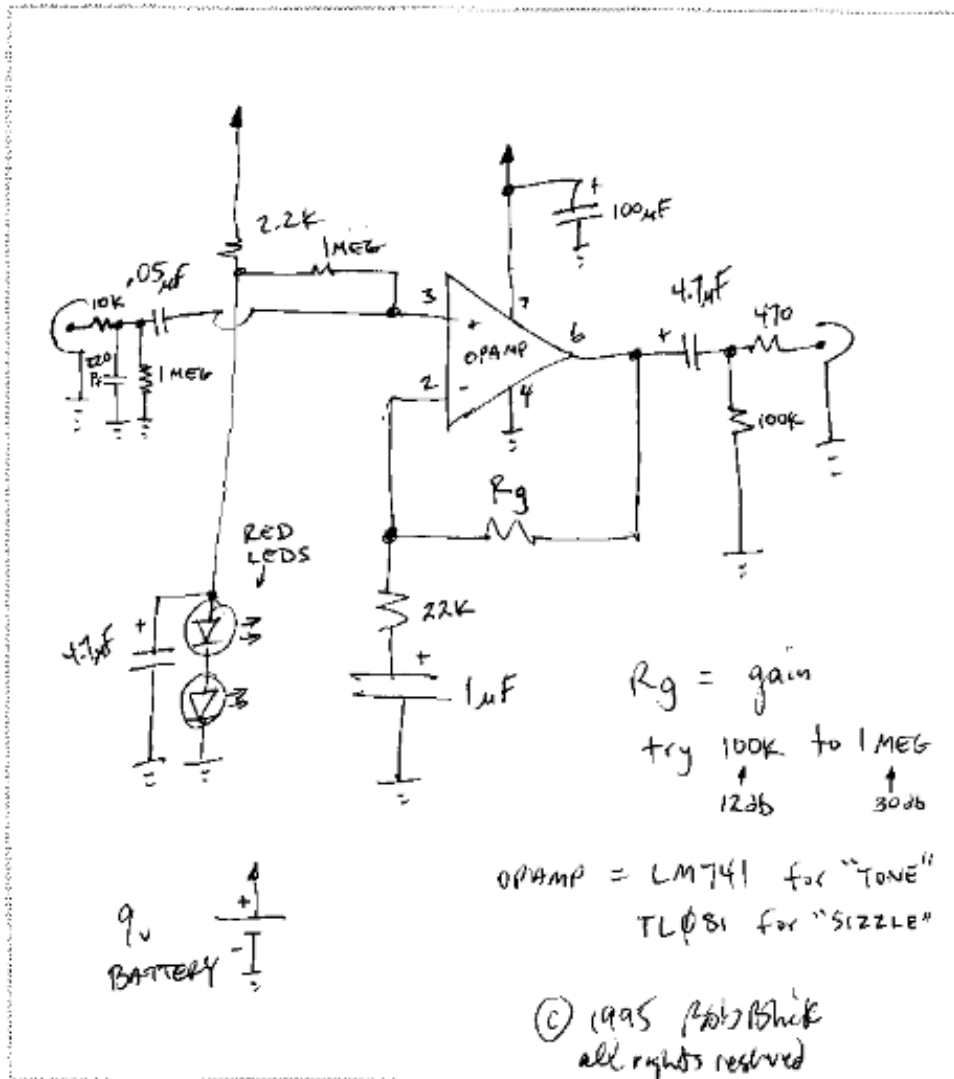



S-ENG-7-REV. 051

PROPIC2 PIC PROGRAMMER

Status: OK

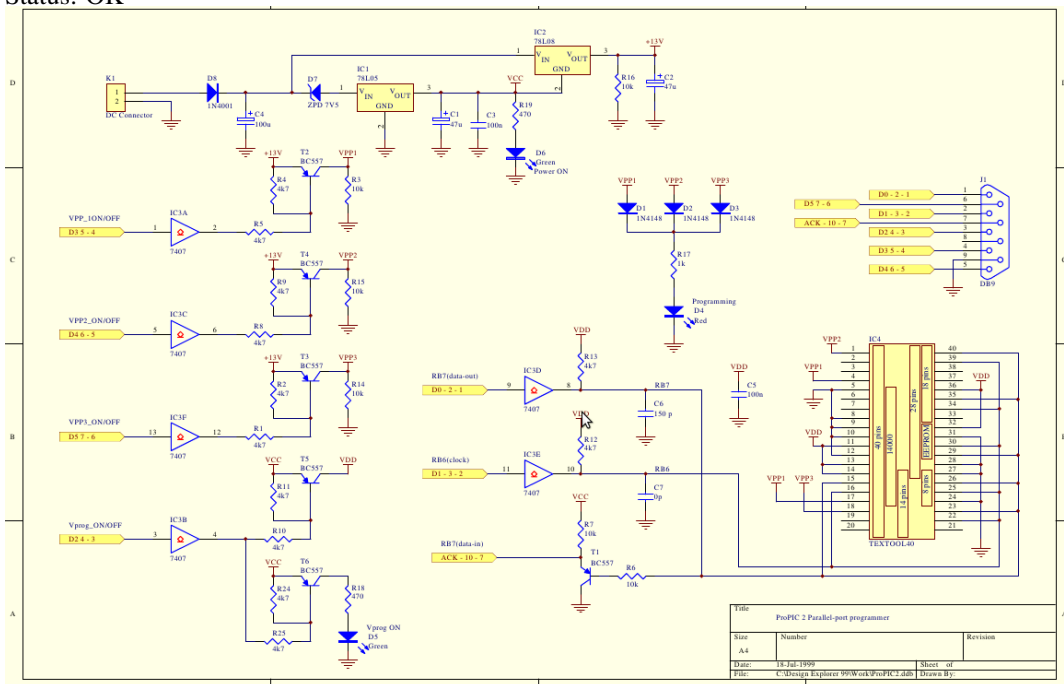

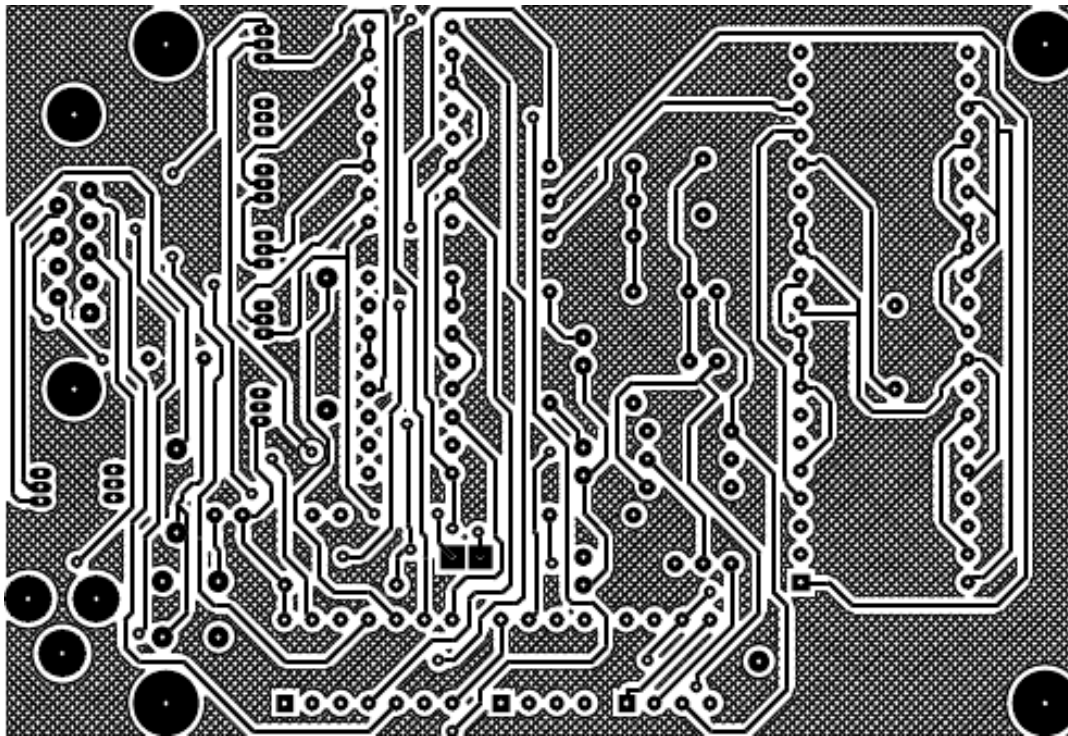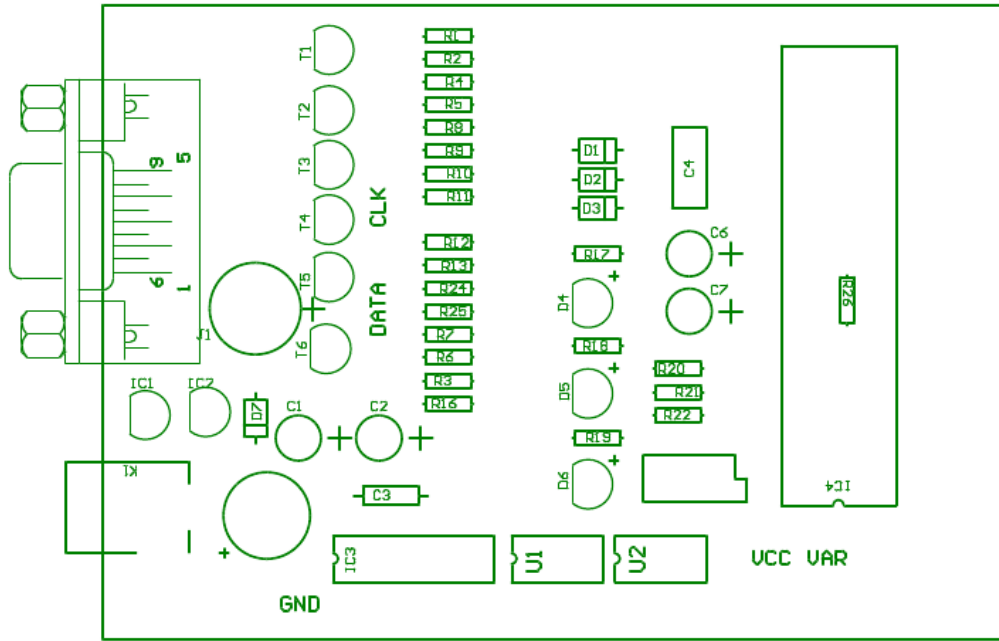

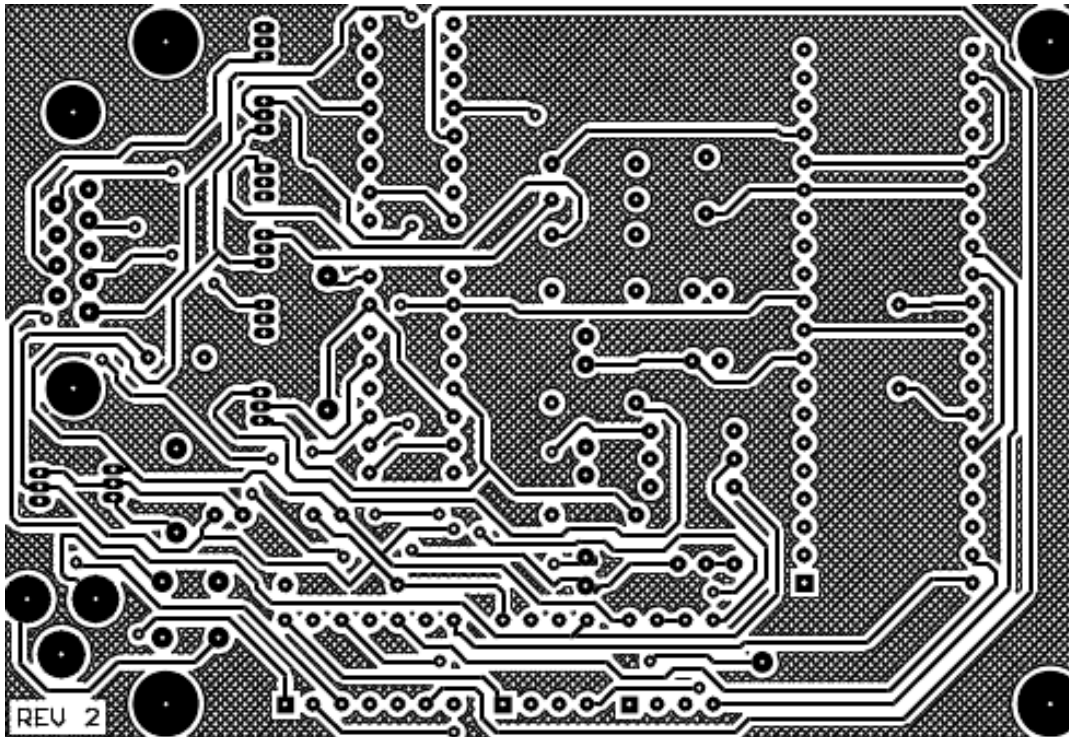

Links:

- <http://www.mpu51.com/propic/propic2.htm>

SERIAL PORT 1WIRE ADAPTER

Status: OK

original design: <http://owfs.org/index.php?page=com-ds9097-passive>

SERIAL PORT LOOPBACK PLUG

Status: OK

It is used for testing the serial port.

Connected pins:

- 1-6-4
- 2-3
- 7-8

27.1 Images



27.2 Sources

original design


Serial port pinout

SERIAL PORT MONITOR

Status: OK





On each signal there is one LED for positive and one LED for negative voltage. It is easy to change connections or connect external parts. Examples: Loop-Back, Null Modem,..

28.1 Schematic

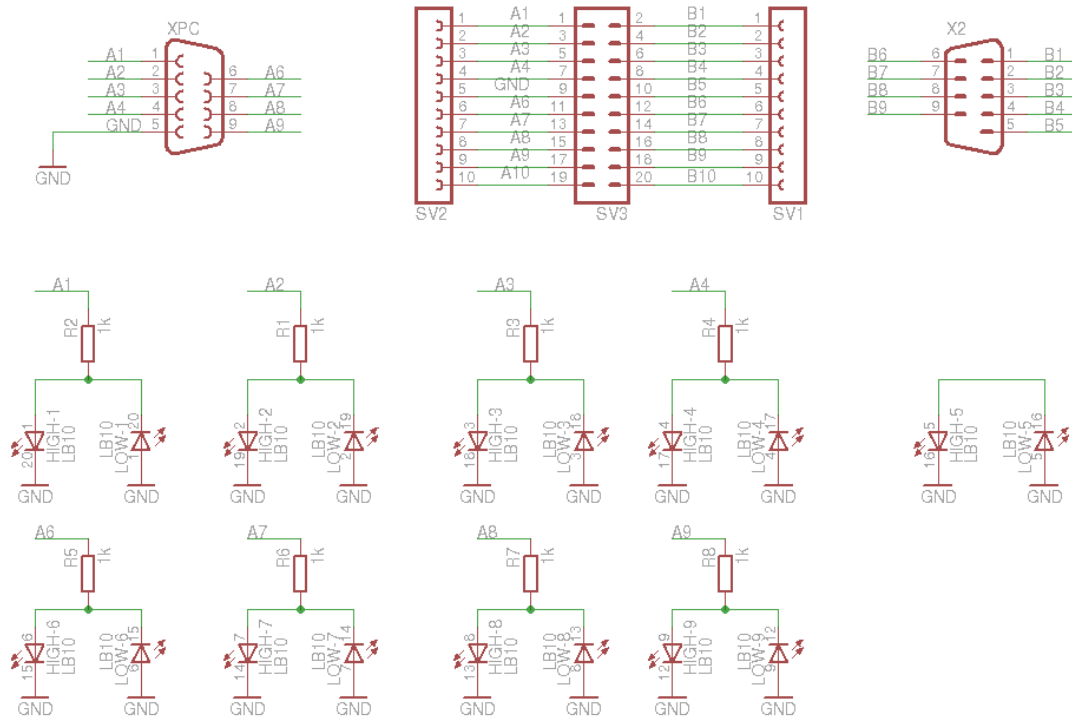

28.2 Board

Normal, bottom mirrored, wires only:

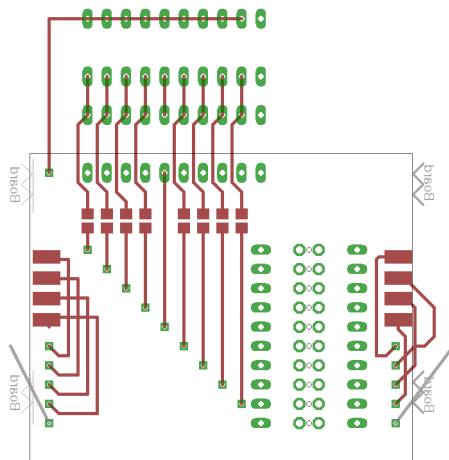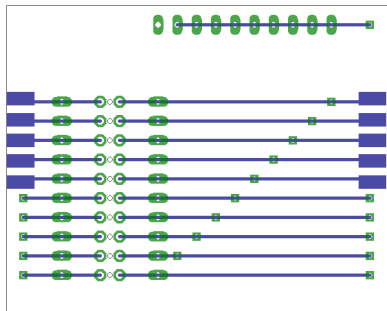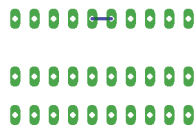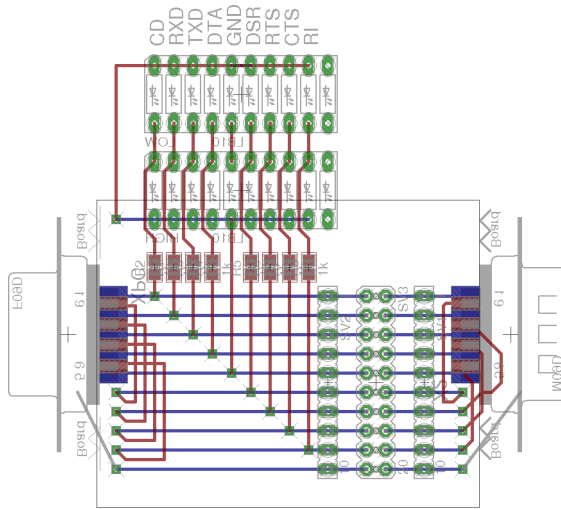


28.3 Partlist

Table 28.1:


part	value	position
HIGH	LB10	(0.75 1.65)
LOW	LB10	(0.75 2.15)
R1	1k	(0.4 1.25)
R2	1k	(0.3 1.25)
R3	1k	(0.5 1.25)
R4	1k	(0.6 1.25)
R5	1k	(0.8 1.25)
R6	1k	(0.9 1.25)
R7	1k	(1 1.25)
R8	1k	(1.1 1.25)
SV1		(1.7 0.65)
SV2		(1.2 0.65)
SV3		(1.45 0.65)
X2		(2.15 0.9)
XPC		(-0.15 0.9)

28.4 3D view


28.4.1 Front

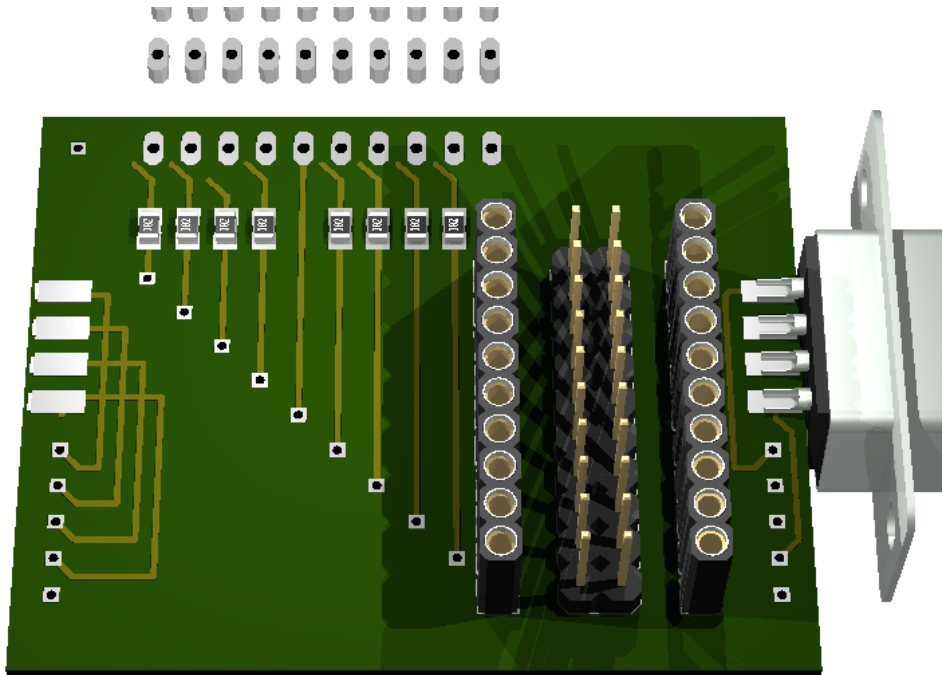


28.4.2 Right side

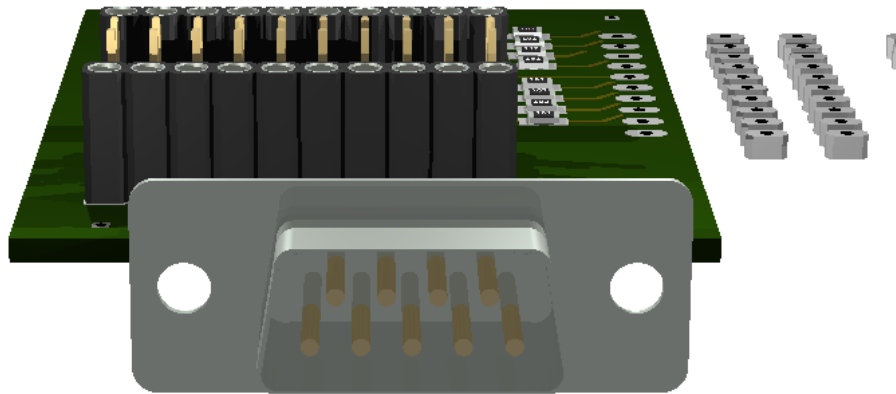


28.4.3 Left side

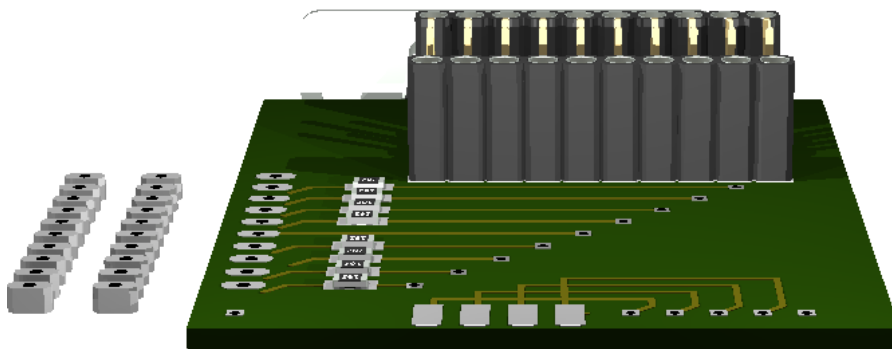


28.4.4 Bottom

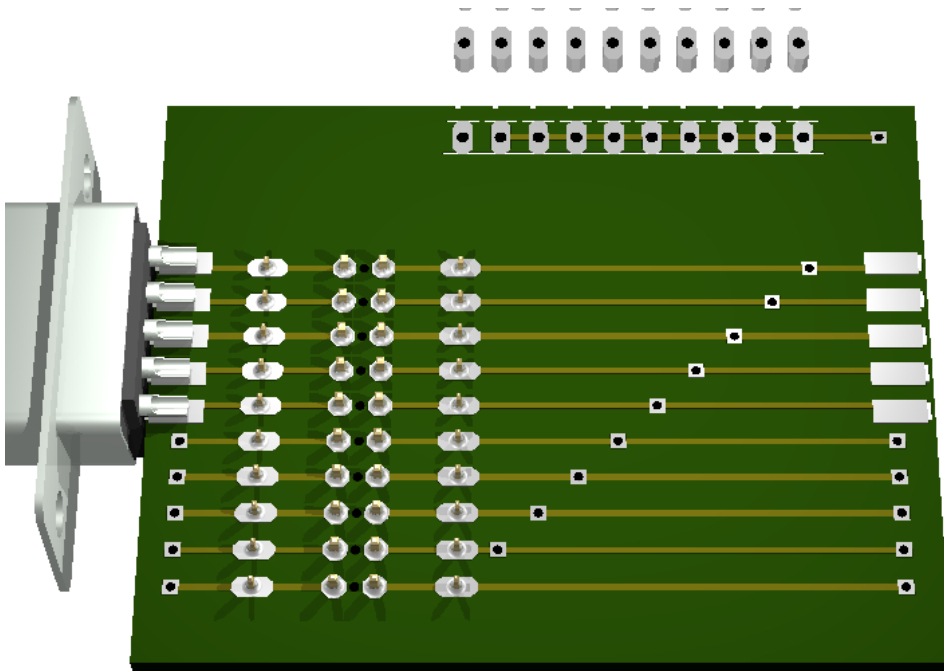

28.5 Images

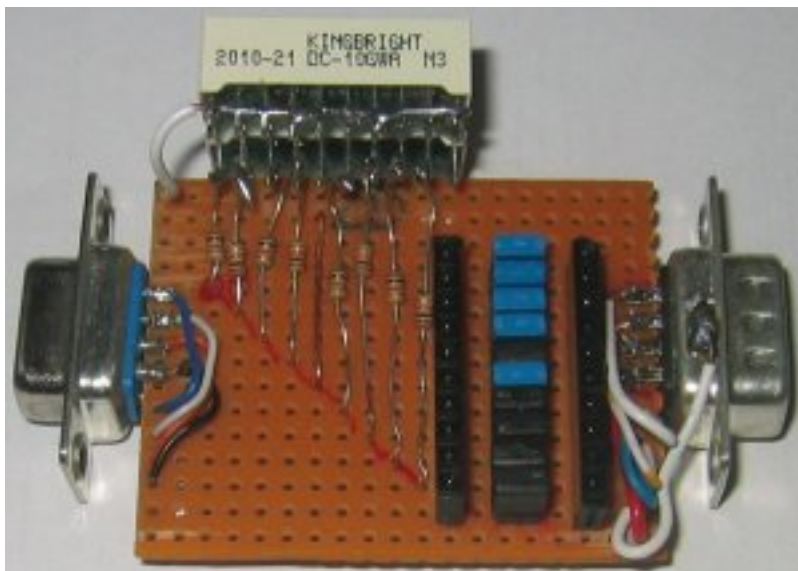


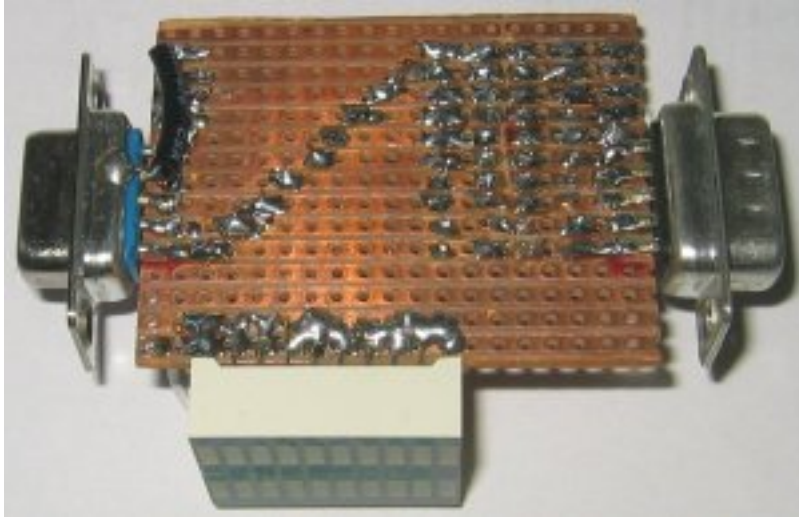


STANDBY KILLER

Status: OK

29.1 Schematic

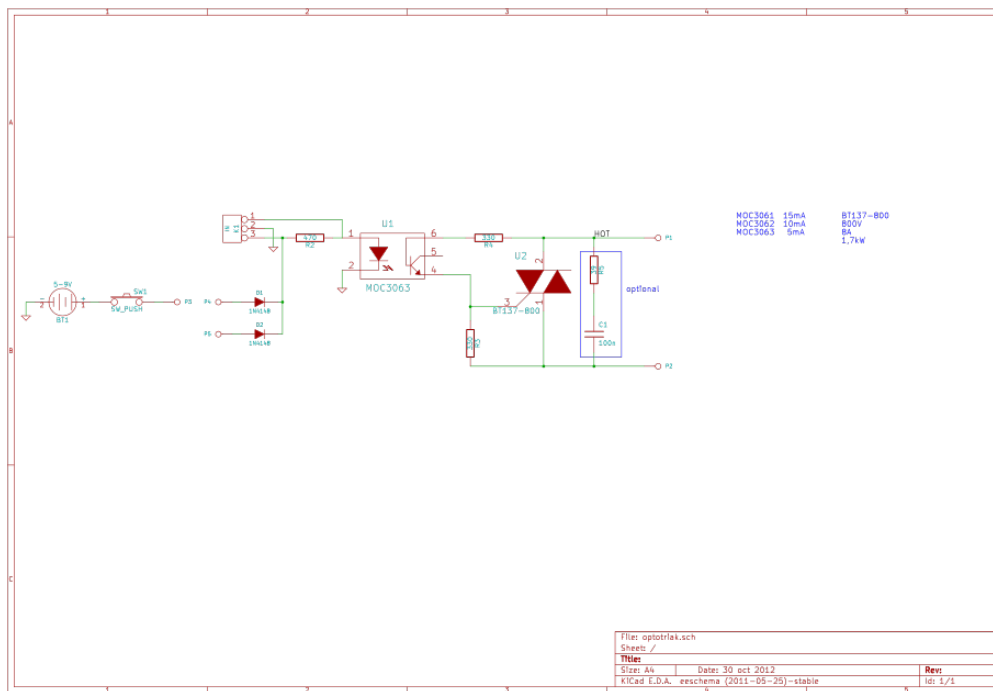

29.2 Board

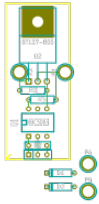

29.3 Sources

based on: <http://www.extremecircuits.net/2010/05/usb-operated-home-appliances.html>

STK200 AVR PROGRAMMER

Status: OK


It is used for programming AVR controller and Arduino compatible boards using the parallel port.


30.1 Test on Ubuntu

checking:


```
$ avrdude -patmega88 -cstk200
avrdude: AVR device initialized and ready to accept instructions
Reading | ##### | 100% 0.00s
avrdude: Device signature = 0x1e930a
avrdude: safemode: Fuses OK
avrdude done. Thank you.
```

30.2 Image

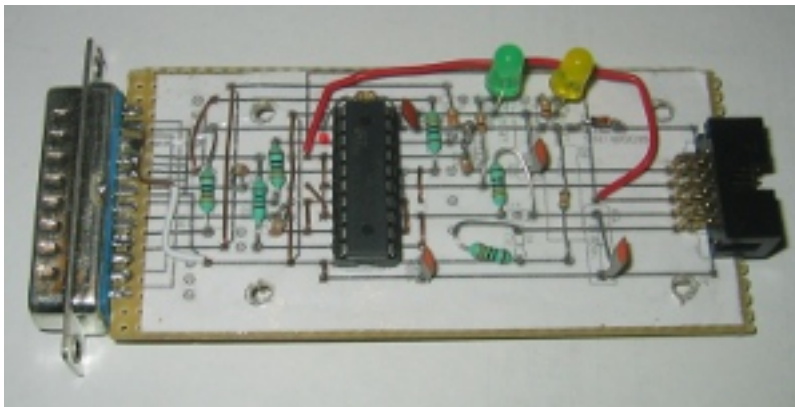

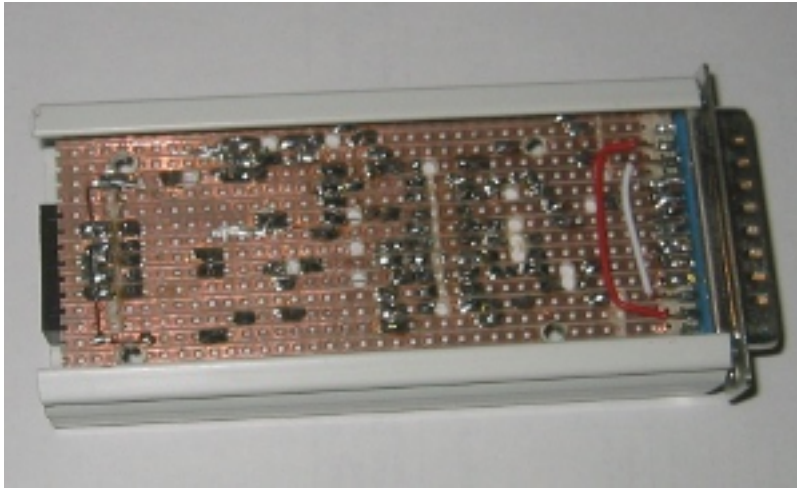


30.3 Schematic

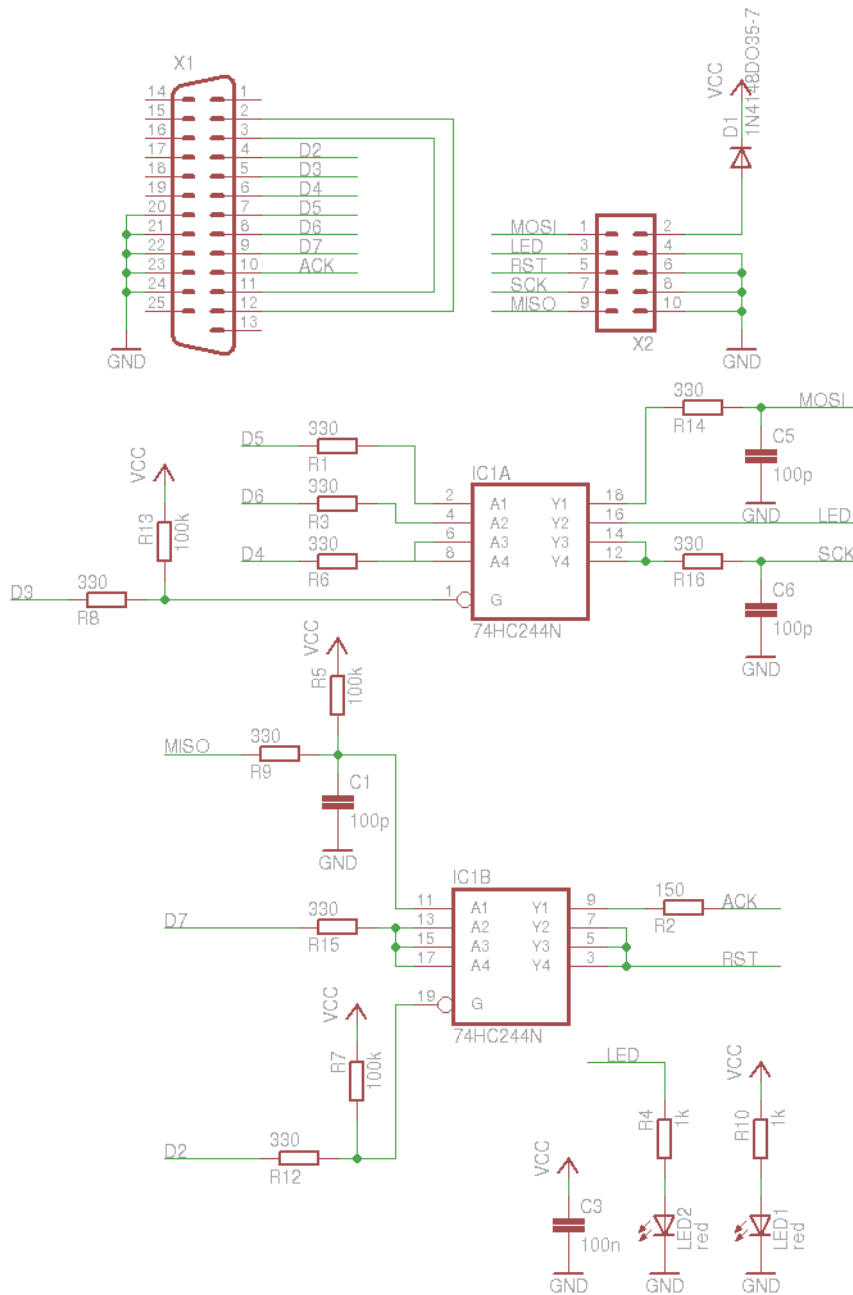

30.4 Board

Normal, bottom mirrored, wires only:

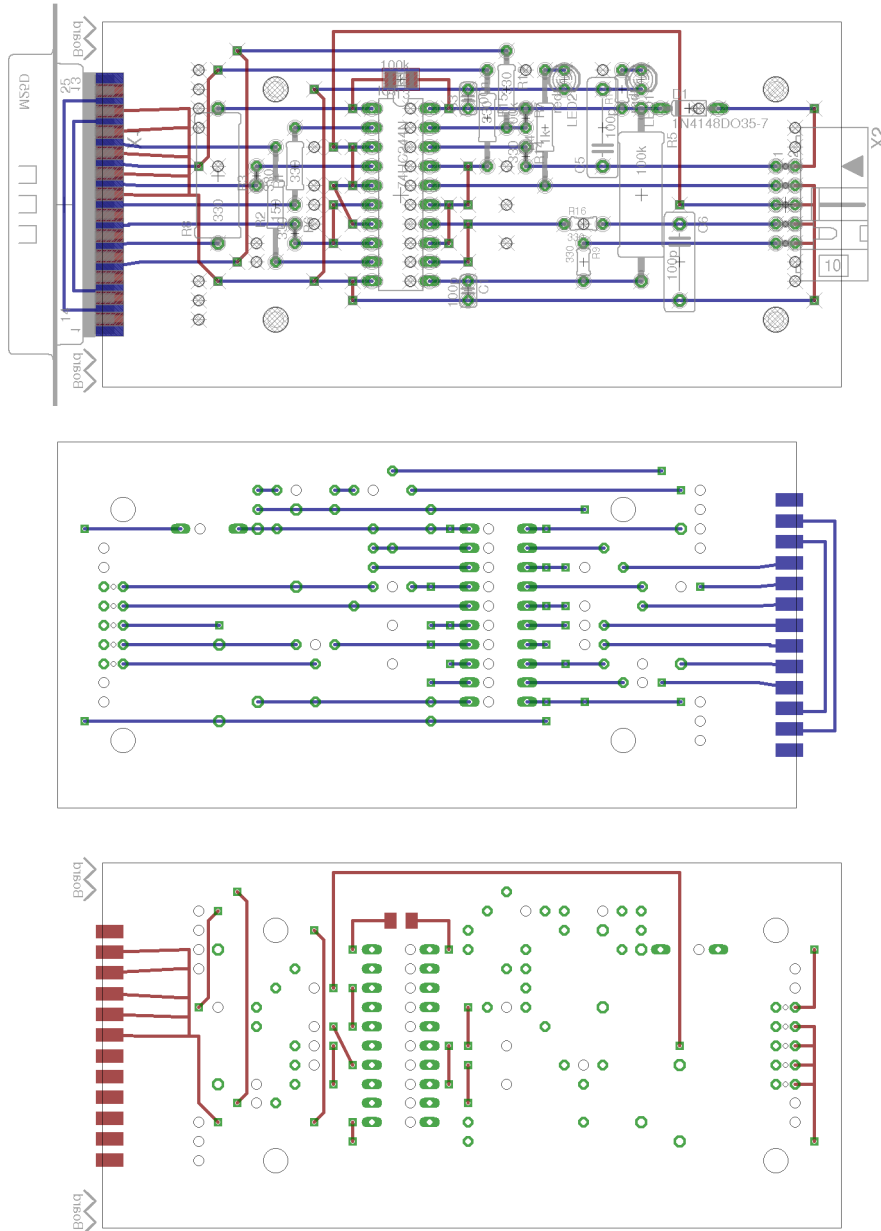


30.5 Partlist

Table 30.1:


part	value	position
C1	100p	(2.3 0.95)
C3	100n	(2.3 1.95)
C5	100p	(3 1.8)
C6	100p	(3.4 1.1)
D1	1N4148DO35-7	(3.45 1.9)
IC1	74HC244N	(1.95 1.45)
LED1	red	(3.2 2.05)
LED2	red	(2.8 2.05)
R1	330	(1.4 1.6)
R2	150	(1.3 1.4)
R3	330	(1.2 1.55)
R4	1k	(2.7 1.8)
R5	100k	(3.2 1.45)
R6	330	(1.4 1.25)
R7	100k	(2.6 1.85)
R8	330	(1 1.55)
R9	330	(2.9 1.1)
R10	1k	(3.1 2)
R12	330	(2.5 2)
R13	100k	(1.95 2.05)
R14	330	(2.6 1.65)
R15	330	(2.4 1.85)
R16	330	(2.9 1.3)
X1		(0.2 1.4)
X2		(3.95 1.4)

30.6 3D view


30.6.1 Front

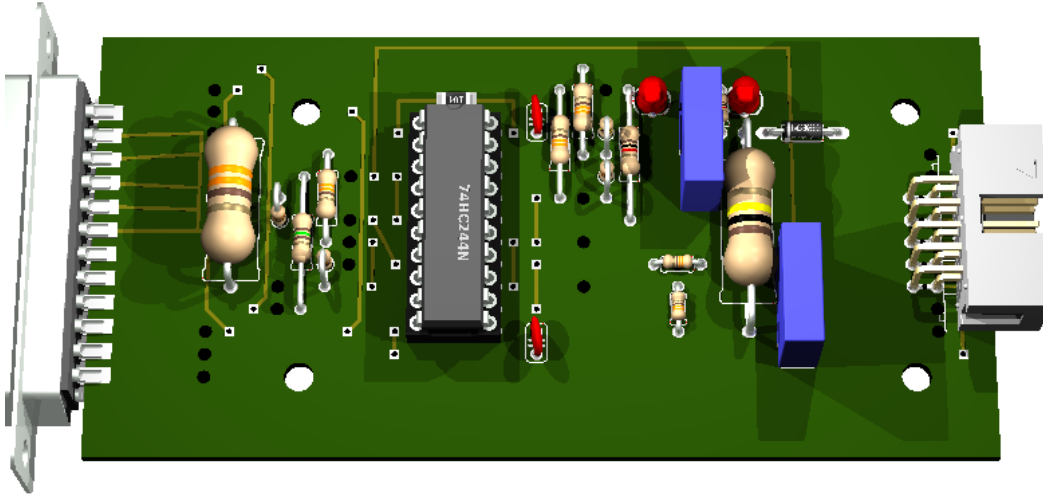


30.6.2 Right side

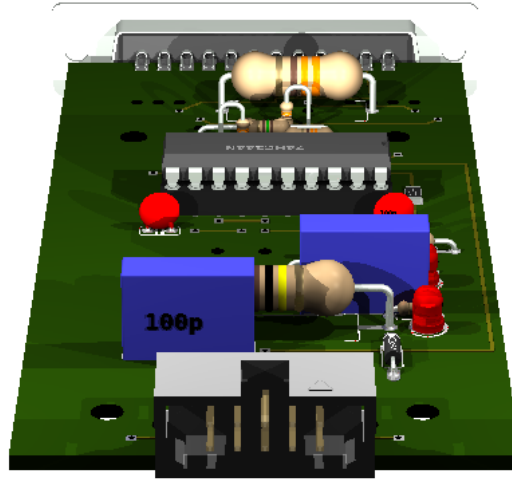

30.6.3 Left side

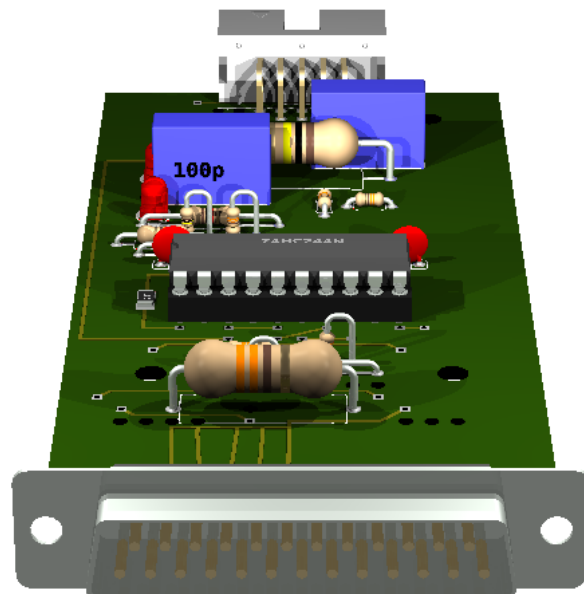

30.6.4 Bottom

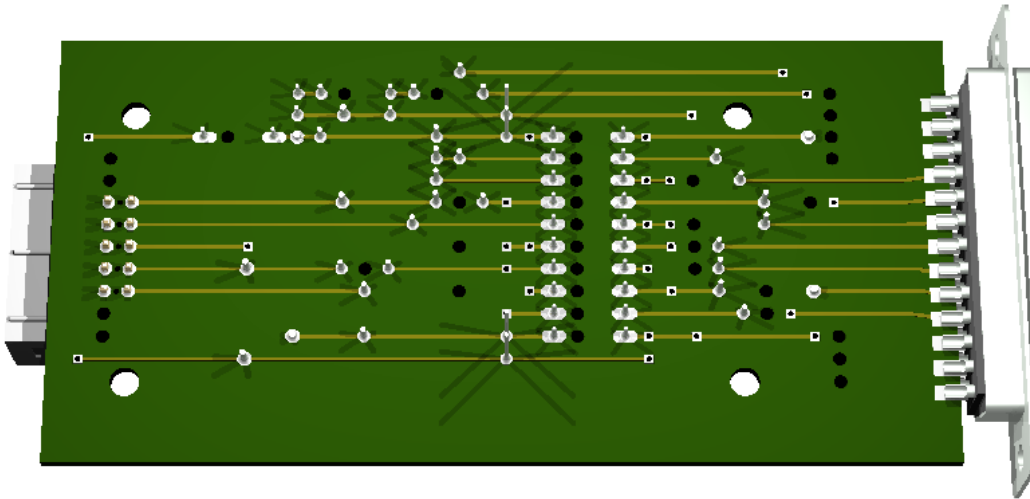

30.7 Sources

original design

Parallel port specification

AVR ISP Header Pinouts

similar designs:

- <http://www.sbprojects.com/projects/stk200/>

USB 1WIRE HUB

Status: OK

Low speed USB device which can handle multiple `1wire` buses. Example program: `onewire_demo.py` under `softusbduino`

Based on `V-USB` hardware.


connections:

function	AVR pin	Arduino pin
1wire	PC0	A0
1wire	PC1	A1
1wire	PC2	A2
1wire	PD5	D5
1wire	PD6	D6
1wire	PD7	D7
USB D-	PD0	D0
USB D+	PD2	D2

V-USB defines:


```
#define USB_CFG_IOPORTNAME    D
#define USB_CFG_DMINUS_BIT    0
#define USB_CFG_DPLUS_BIT     2
```


31.1 Schematic

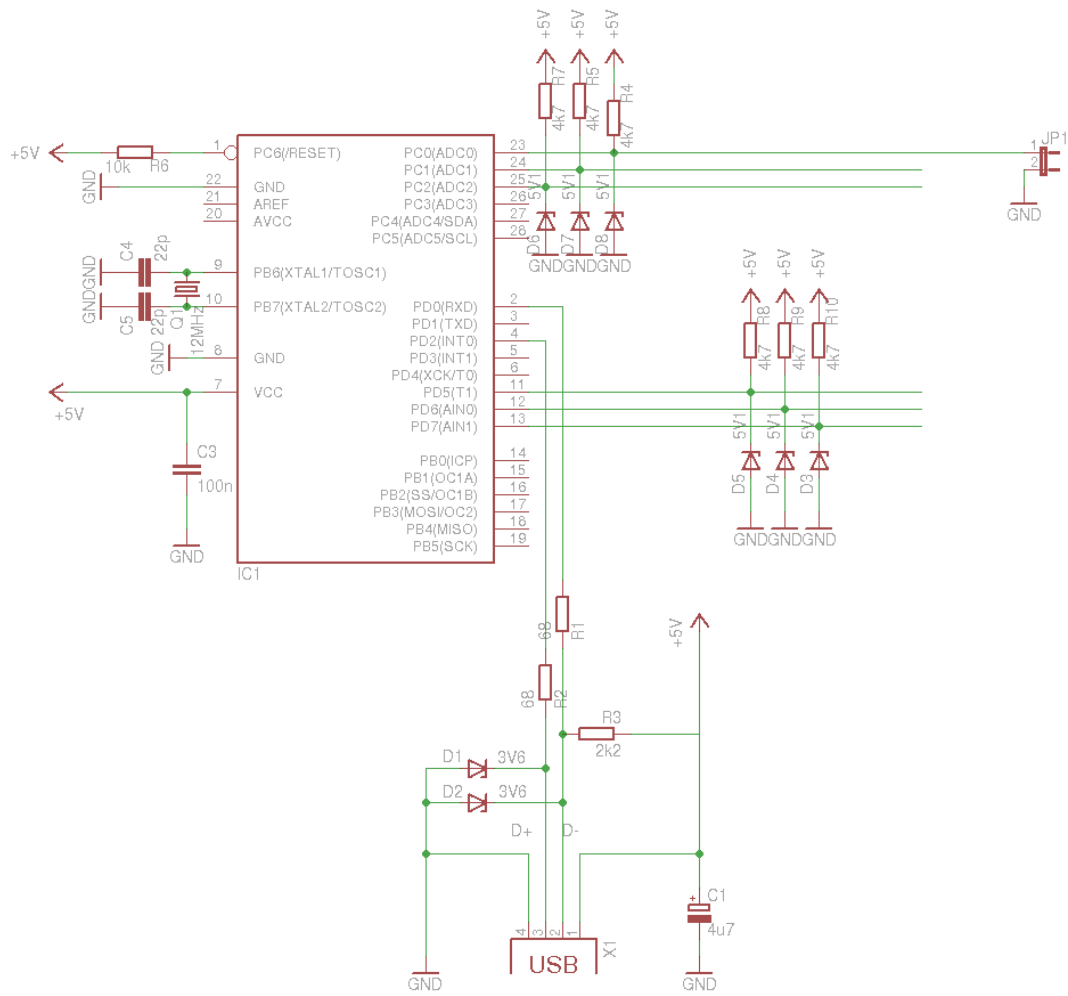

31.2 Board

Normal, bottom mirrored, wires only:

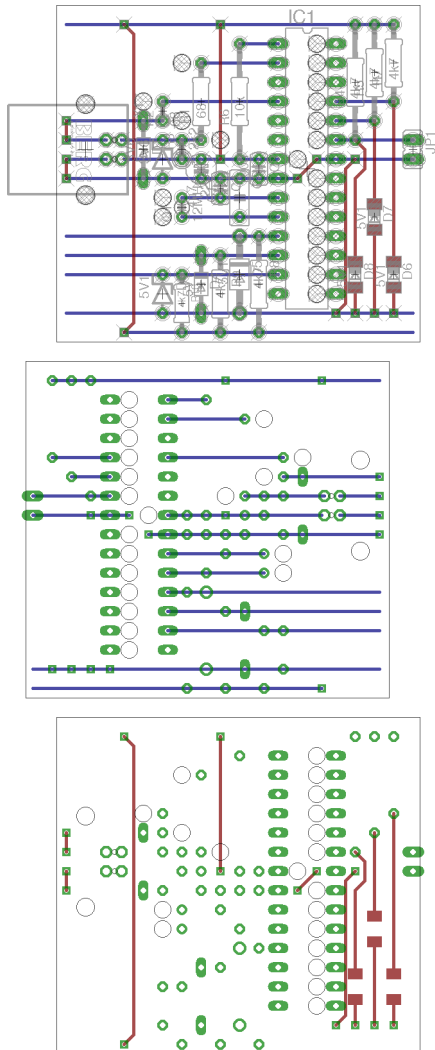


31.3 Partlist

Table 31.1:


part	value	position
C1	4u7	(0.9 1.05)
C3	100n	(1.2 1.05)
C4	22p	(1 0.95)
C5	22p	(1.1 0.9)
D1	3V6	(0.6 1.15)
D2	3V6	(0.7 1.1)
D3	5V1	(0.7 0.4)
D4	5V1	(0.9 0.45)
D5	5V1	(1.1 0.5)
D6	5V1	(1.9 0.5)
D7	5V1	(1.8 0.8)
D8	5V1	(1.7 0.5)
IC1		(1.45 1.05)
JP1		(2 1.15)
Q1	12MHz	(0.8 0.85)
R1	68	(0.9 1.4)
R2	68	(0.7 1.35)
R3	2k2	(0.8 1.15)
R4	4k7	(1.7 1.5)
R5	4k7	(1.8 1.55)
R6	10k	(1.1 1.4)
R7	4k7	(1.9 1.6)
R8	4k7	(1.2 0.45)
R9	4k7	(1 0.4)
R10	4k7	(0.8 0.35)
X1		(0.3 1.15)

31.4 3D view


31.4.1 Front

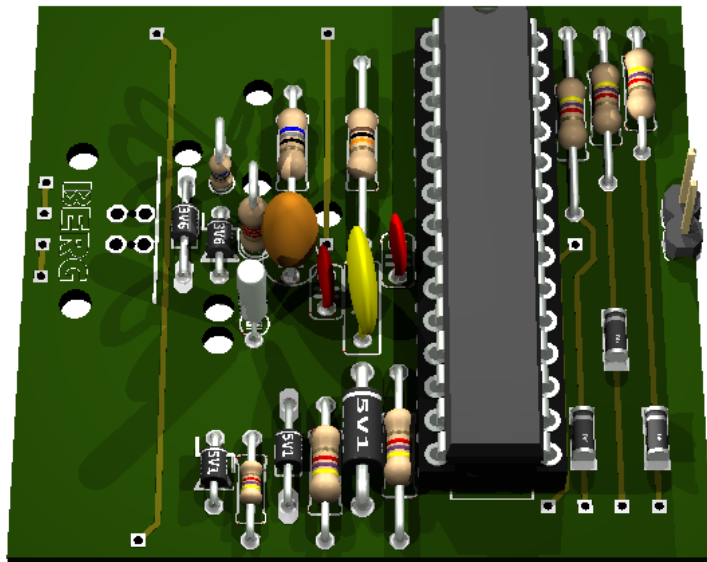


31.4.2 Right side

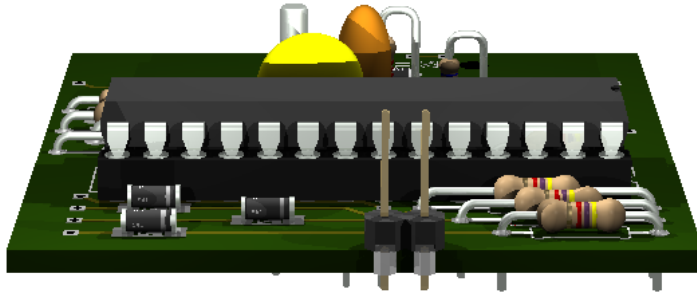

31.4.3 Left side

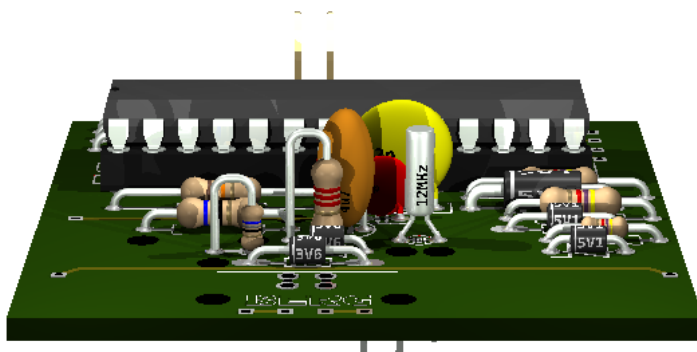

31.4.4 Bottom

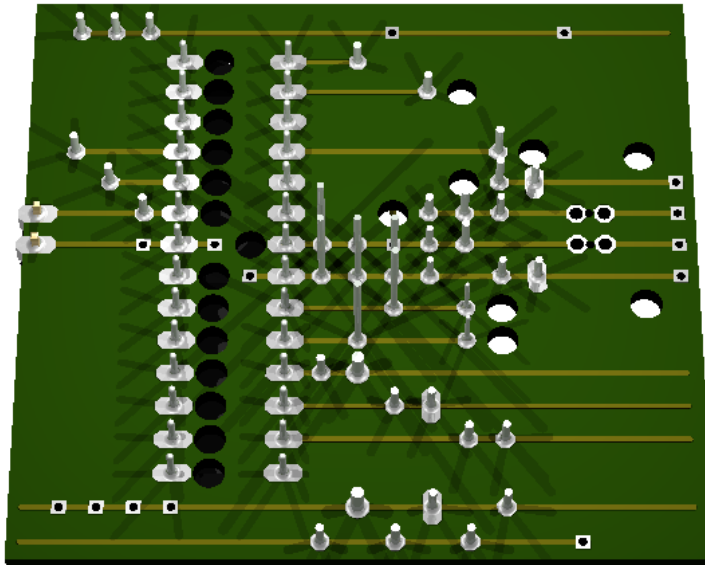

USB TRICKLE CHARGER

Status: OK

Charging current: 50 mA

USB port power is max 500 mA -> 9 charger can be connected to one USB port

32.1 Power dissipation

LED

- current = 15 mA
- power = 30 mW

R4

- current = 35 mA
- power = 60 mW

Transistor


- current = 50 mA
- power = 100 mW

32.2 Charge time

$$T = C * 1.5 / 50\text{mA}$$

Capacity	current	time(h)	time(d)
1000 mAh	C/20	30h	1.25d
2000 mAh	C/40	60h	2.5d
3000 mAh	C/60	90h	3.75d

32.3 Schematic

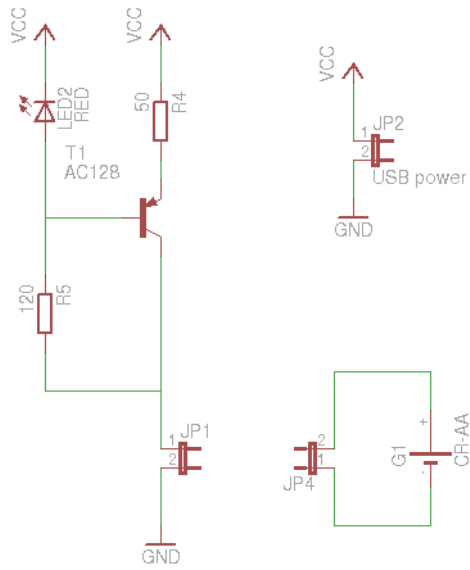


32.4 Sources

Based on this design: <http://www.extremecircuits.net/2009/10/low-cost-universal-battery-charger.html>

USB LED

Status: OK

It is used for testing USB power.

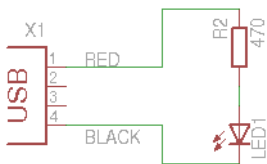

USBASP AVR PROGRAMMER

Status: OK

It is used for programming AVR controller and Arduino compatible boards using the USB port.

firmware, design: <http://www.fischl.de/usbasp/>

USBasp is based on V-USB (<http://www.obdev.at/products/vusb/index.html>)

34.1 V-USB hardware recommendation

only difference to USBasp: 1.5 k Ω pull-up resistor

<http://vusb.wikidot.com/hardware>

“Solution B: Level conversion on D+ and D- Level conversion with Zener diodes.

Instead of reducing the AVR’s power supply, we can limit the output voltage on D+ and D- with Zener diodes. We recommend 3.6 V low power types, those that look like 1N4148 (usually 500 mW or less). Low power types are required because they have less capacitance and thus cause less distortion on the data lines. And 3.6 V is better than 3.3 V because 3.3 V diodes yield only ca. 2.7 V in conjunction with an 1.5 k Ω (or more exactly 10 k Ω) pull-up resistor. With 3.3 V diodes, the device may not be detected reliably.

If you use Zener diodes for level conversion, please measure the voltage levels to make sure that the diodes you have chosen match the requirements.

Advantages of the Zener diode approach:

- Low cost.
- Easy to obtain.
- Entire design can be at 5 V.
- AVR can be clocked at high rates.

Disadvantages:

- Not a clean solution, a compromise between all parameters must be found.
- Zener diodes come with a broad range of characteristics, especially at low currents, results may not be reproducible.
- High currents when sending high-level.
- High level is different for signaling and in idle state because signaling uses high currents to drive the diodes while idle state is driven by a 1.5 k Ω pull-up resistor.”

34.2 Makefile

Tested with atmega88. Makefile settings:

```
TARGET=atmega88
HFUSE=0xdd
LFUSE=0xef
```

34.3 Test on Ubuntu

checking:

```
$ lsusb |grep -i 16c0:05dc
Bus 003 Device 006: ID 16c0:05dc VOTI shared ID for use with libusb
```

```
$ ls -l /dev/bus/usb/003/006
crw-rw-r-- 1 root root 189, 261 2011-11-05 10:31 /dev/bus/usb/003/006
```

```
$ avrdude -patmega88 -cusbasp
avrdude: Warning: cannot query manufacturer for device: error sending control message: Operation
avrdude: error: could not find USB device "USBasp" with vid=0x16c0 pid=0x5dc
```

The permission should be changed:

```
$sudo nano /etc/udev/rules.d/60-objdev.rules
```

add this line:

```
ATTRS{idVendor}=="16c0", ATTRS{idProduct}=="05dc", GROUP="users", MODE="0666"
```

update rules:

```
$sudo udevadm trigger
```

checking again:

```
$ ls -l /dev/bus/usb/003/006
crw-rw-rw- 1 root users 189, 261 2011-11-05 10:33 /dev/bus/usb/003/006
```

```
$ avrdude -patmega88 -cusbasp
avrdude: error: programm enable: target doesn't answer. 1
avrdude: initialization failed, rc=-1
      Double check connections and try again, or use -F to override
      this check.
avrdude done. Thank you.
```

Permission is OK now.

Testing with connected controller:

```
$ avrdude -patmega88 -cusbasp

avrdude: AVR device initialized and ready to accept instructions


Reading | ##### | 100% 0.01s

avrdude: Device signature = 0x1e930a

avrdude: safemode: Fuses OK


avrdude done. Thank you.
```

34.4 Schematic

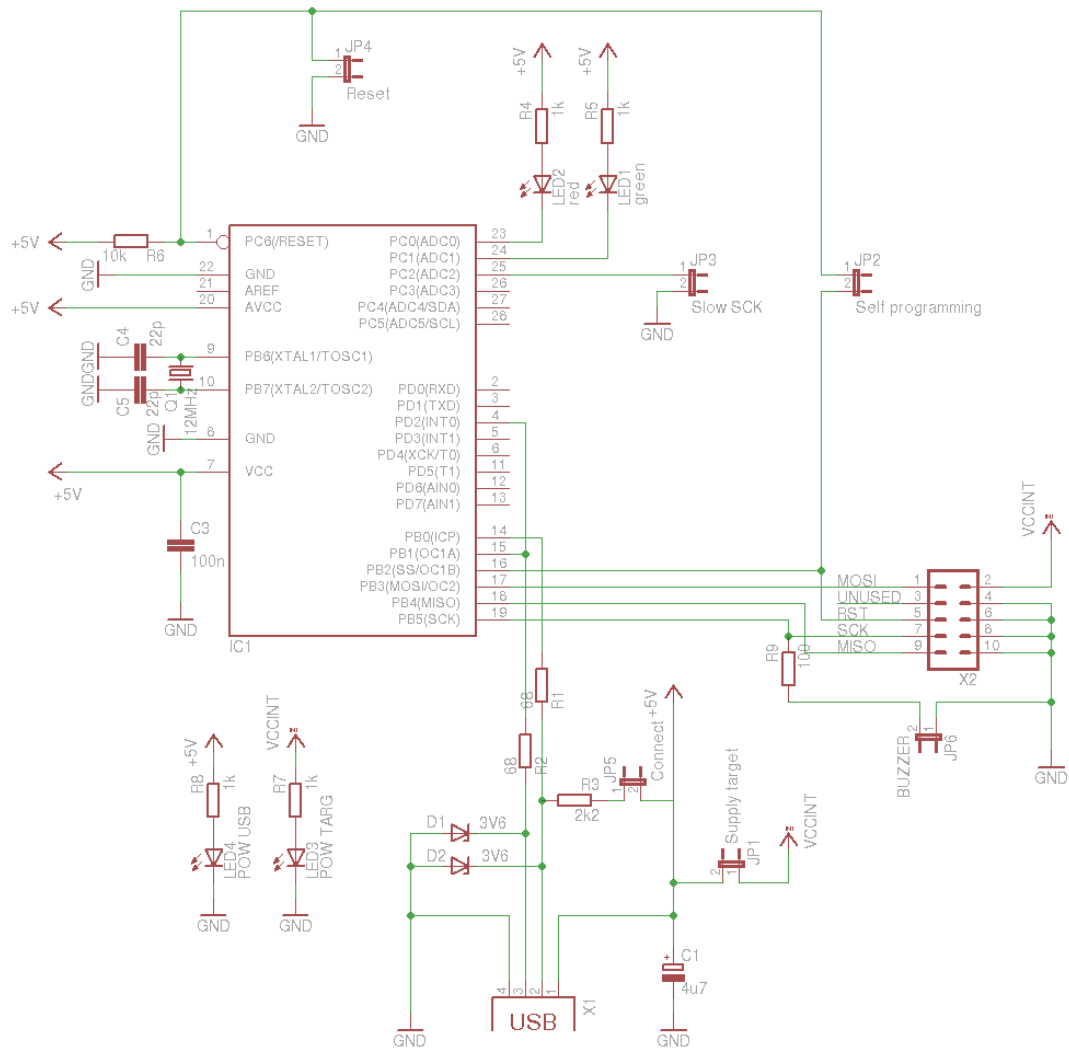

34.5 Board

Normal, bottom mirrored, wires only:

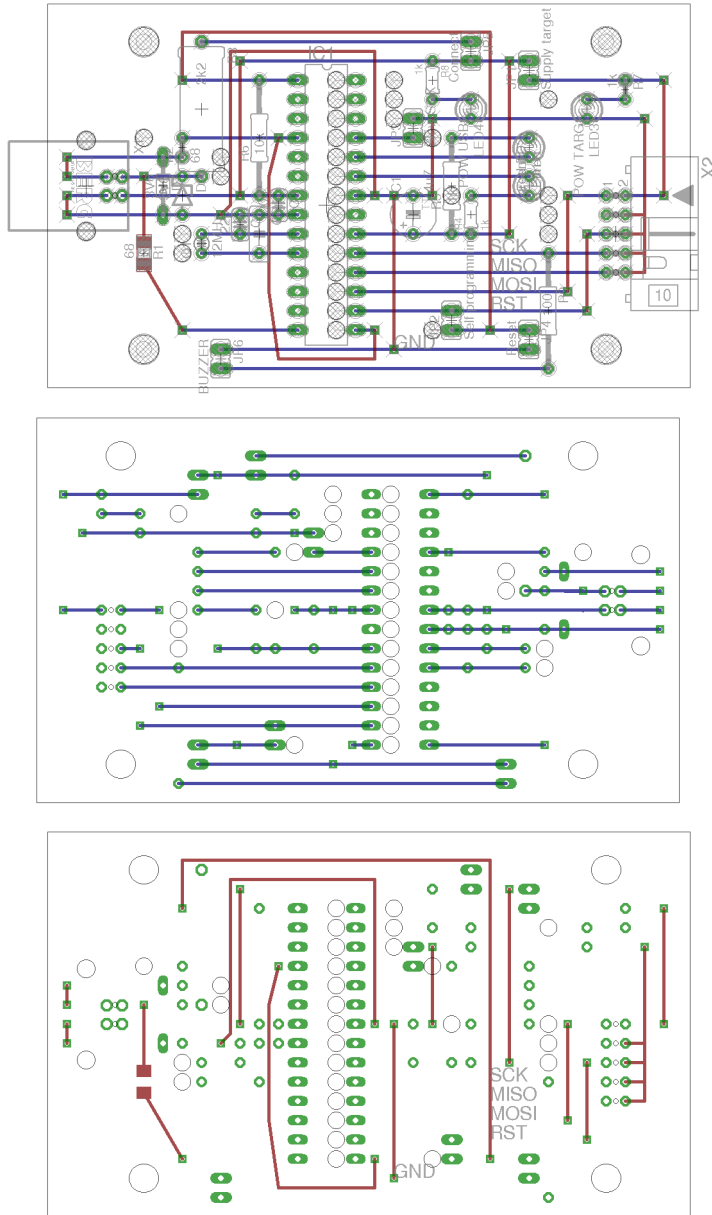


34.6 Partlist

Table 34.1:


part	value	position
C1	4u7	(2.4 0.8)
C3	100n	(1.7 0.85)
C4	22p	(1.5 0.75)
C5	22p	(1.6 0.7)
D1	3V6	(1.1 0.95)
D2	3V6	(1.2 0.9)
IC1		(1.95 0.85)
JP1	Supply target	(3 1.55)
JP2	Self programming	(2.6 0.25)
JP3	Slow SCK	(2.4 1.25)
JP4	Reset	(3 0.15)
JP5	Connect	(2.7 1.65)
JP6	BUZZER	(1.4 0.05)
LED1	green	(3 1.15)
LED2	red	(3 0.95)
LED3	POW TARG	(3.3 1.35)
LED4	POW USB	(2.7 1.35)
Q1	12MHz	(1.3 0.65)
R1	68	(1 0.6)
R2	68	(1.2 1.15)
R3	2k2	(1.3 1.35)
R4	1k	(2.7 0.8)
R5	1k	(2.6 0.95)
R6	10k	(1.6 1.2)
R7	1k	(3.5 1.45)
R8	1k	(2.5 1.5)
R9	100	(3.1 0.3)
X1		(0.7 0.95)
X2		(3.45 0.7)

34.7 3D view


34.7.1 Front

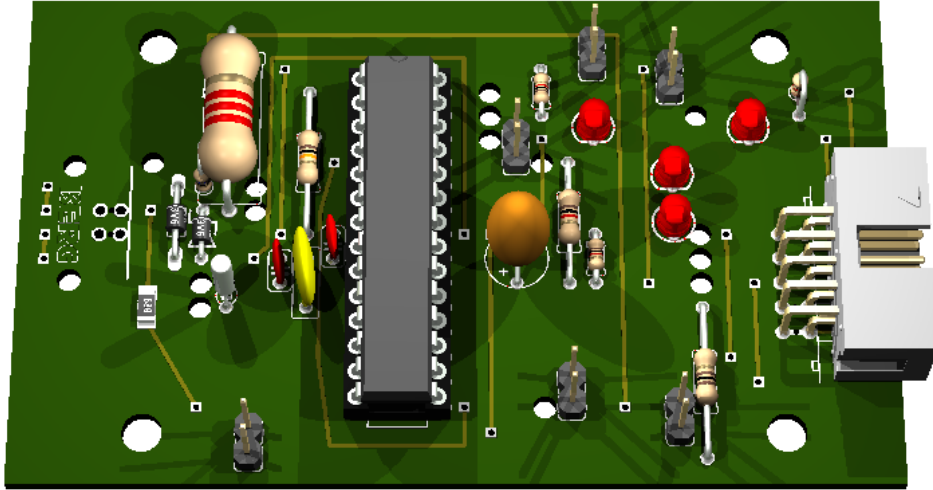


34.7.2 Right side

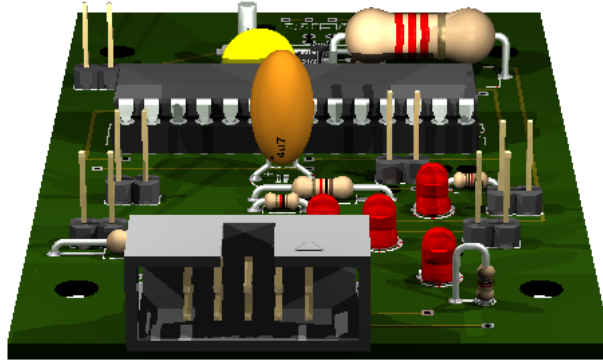

34.7.3 Left side

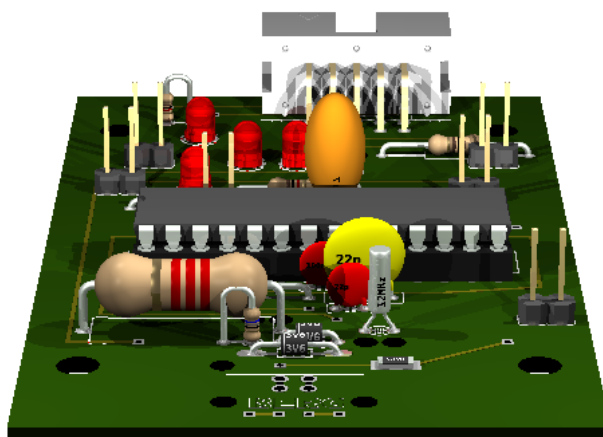

34.7.4 Bottom

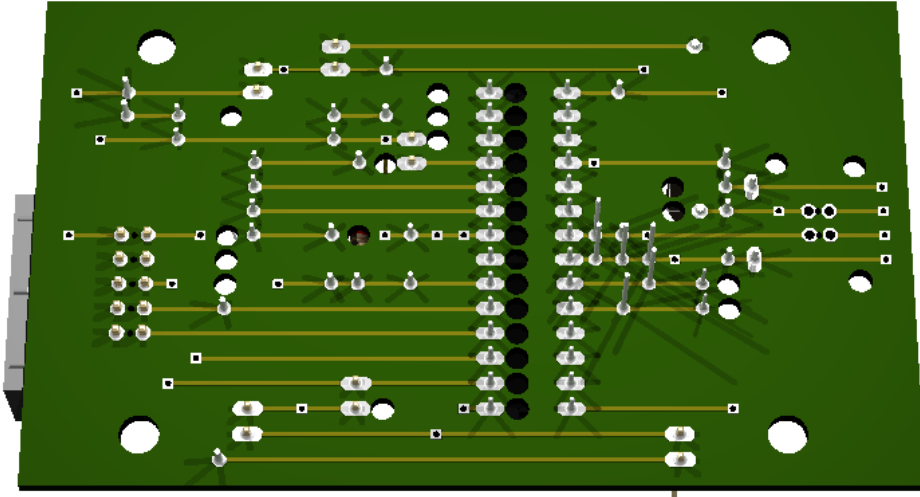

34.8 Reset

To reset on Ubuntu:

```
#!/usr/bin/env python
import logging
import usb.core
logging.basicConfig(level=logging.DEBUG)
import fcntl

ID_VENDOR = 0x16c0
ID_PRODUCT = 0x05dc
USBDEVFS_RESET = 21780

def find():
    print("searching for device (%x:%x)" % (ID_VENDOR, ID_PRODUCT))
    dev = usb.core.find(idVendor=ID_VENDOR,
                        idProduct=ID_PRODUCT,
                        )
    if not dev:
        print("device not found")
    return dev

def usbstr(i):
```

```
s = str(i)
s = '000'[0:3 - len(s)] + s
return s

def usbfs_filename(dev):
    return '/dev/bus/usb/%s/%s' % (usbstr(dev.bus), usbstr(dev.address))

def reset1(dev):
    fname = usbfs_filename(dev)
    print("Resetting USB device %s" % fname)
    with open(fname, 'w') as fd:
        rc = fcntl.ioctl(fd, USBDEVFS_RESET, 0)
        if (rc < 0):
            print("Error in ioctl")
    print("OK")

def reset2(dev):
    dev.reset() # not working

dev = find()
if dev:
    reset1(dev)
```

34.9 Sources

original design

AVR ISP Header Pinouts

similar projects:


- <http://lategahn.2log.de/index.php?USBASP-Stripboard-layout>

WIRE BENDING TOOL

Status: OK


It is used for bending wires.

35.1 Image

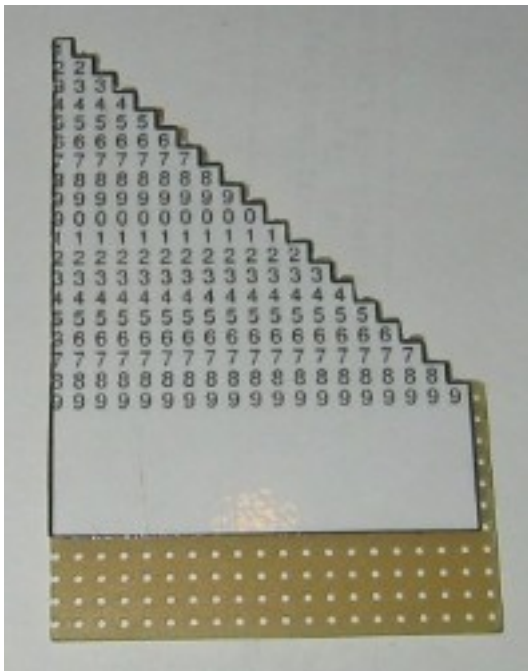


35.2 Board

Normal:

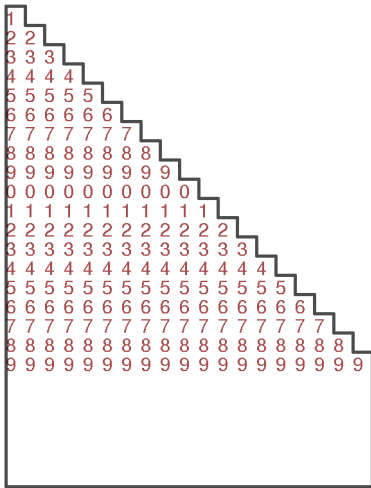

35.3 3D view

35.3.1 Front

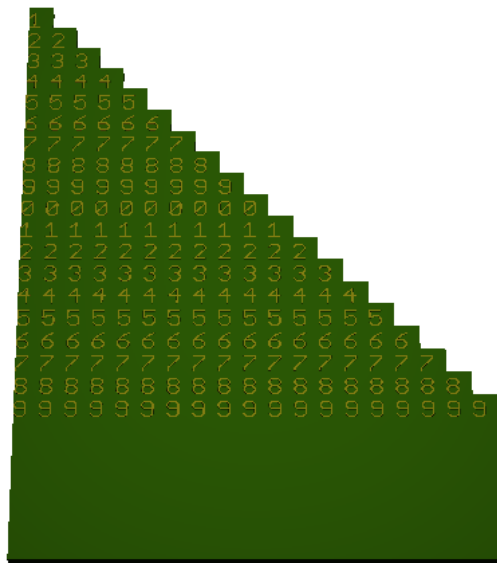

35.3.2 Right side




WIRE DETECTOR

Status: OK

It is used for detecting mains wire.




Based on this design: http://www.edn.com/article/511304-Detect_live_ac_mains_lines.php

36.1 Schematic

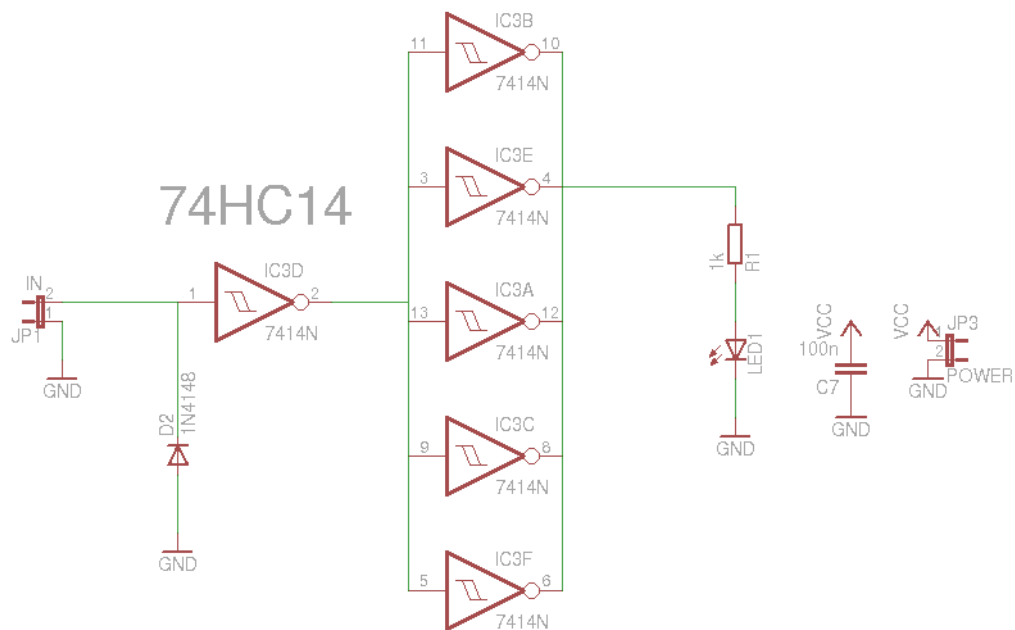

36.2 Board

Normal, bottom mirrored, wires only:

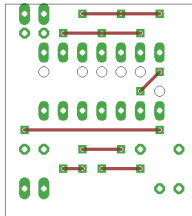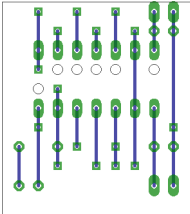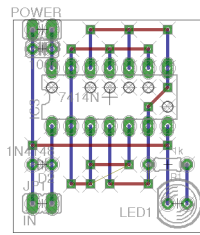


36.3 Partlist

Table 36.1:


part	value	position
C7	100n	(0.85 1.9)
D2	1N4148	(0.85 1.3)
IC3	7414N	(1.2 1.65)
JP1	IN	(0.85 1.1)
JP3	POWER	(0.85 2)
LED1		(1.55 1.1)
R1	1k	(1.5 1.3)

36.4 3D view


36.4.1 Front

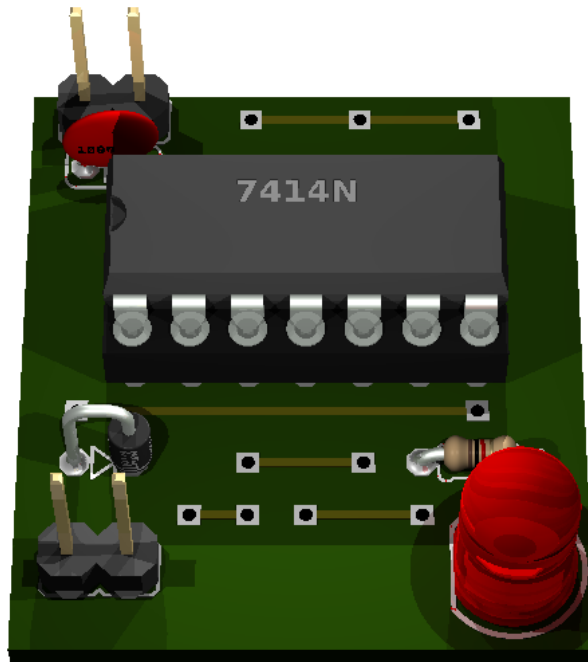


36.4.2 Right side

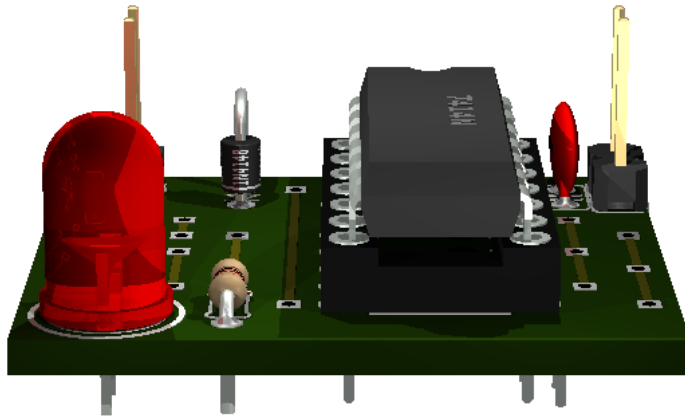

36.4.3 Left side

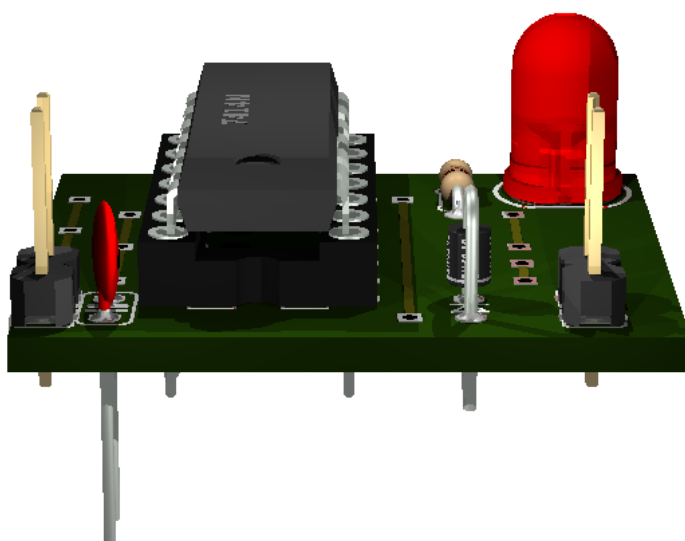

36.4.4 Bottom

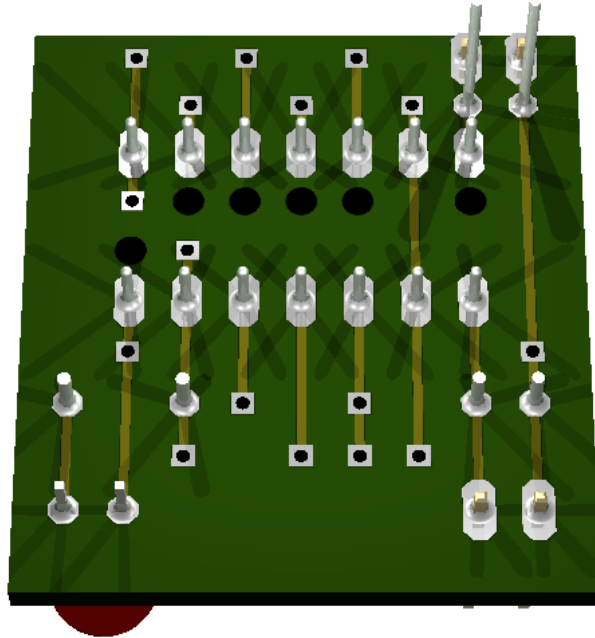

36.5 Sources

original design